



CT Verilog Series

Verilog Overview Part 5

Sequential Blocks

黃稚存

Chih-Tsun Huang

cthuang@cs.nthu.edu.tw



國立清華大學
資訊工程學系

聲明

- ◎ 本課程之內容 (包括但不限於教材、影片、圖片、檔案資料等)，僅供修課學生個人合理使用，非經授課教師同意，不得以任何形式轉載、重製、散布、公開播送、出版或發行本影片內容 (例如將課程內容放置公開平台上，如 Facebook, Instagram, YouTube, Twitter, Google Drive, Dropbox 等等)。如有侵權行為，需自負法律責任。

Outline


- ◎ Sequential Blocks
- ◎ Sequential Example:
4-bit Sequential Counter
- ◎ Summary

- ◎ Part 4 Recap
 - ◆ Combinational Blocks
 - ◆ Combinational Examples
 - ◆ Module Instantiation
 - ◆ Hierarchical Design Style

Sequential Blocks

Sequential Circuits

- ⦿ A sequential circuit consists of a **combinational circuit** to which **storage elements (state registers)** are connected to form a **feedback path**
 - ◆ Binary information stored in the memory elements at any given time defines the **state** of the sequential circuit.
 - ◆ (primary inputs, present state) → (primary outputs, next state)
 - ◆ The behavior is specified by a **time sequence** of inputs and internal states.

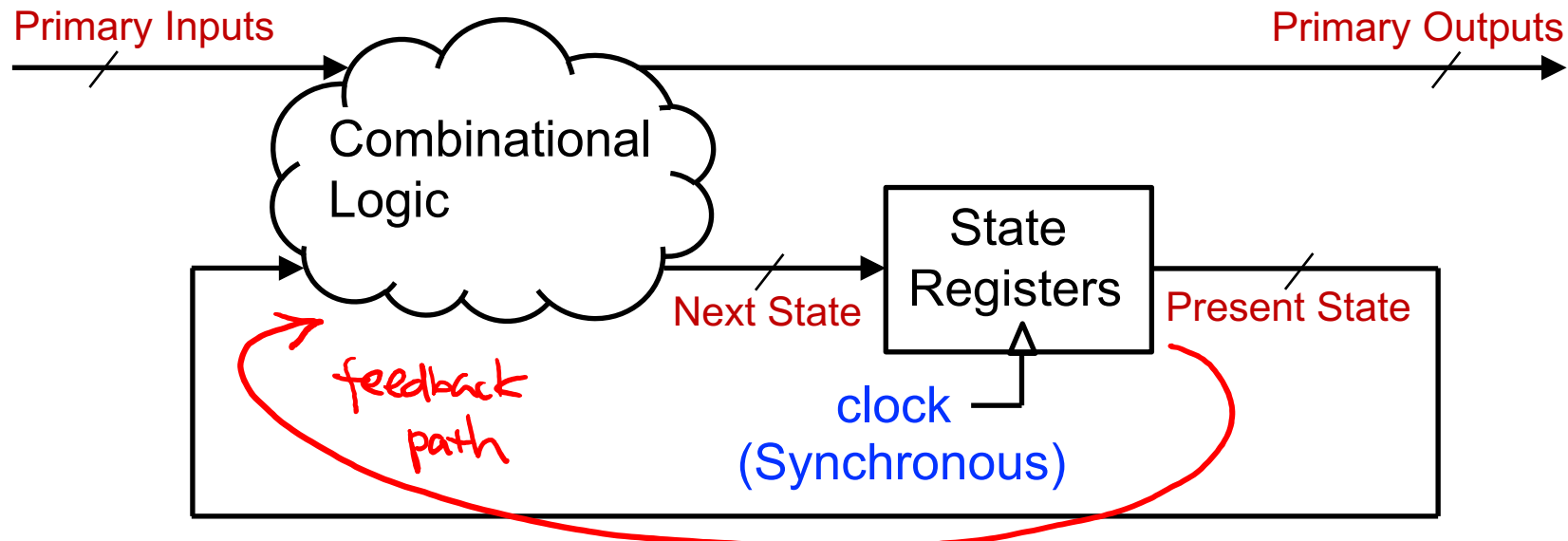

Synchronous vs. Asynchronous Sequential Circuits

⦿ Synchronous

- ◆ Behavior is defined from the input signals at *discrete instants* of time
- ◆ Clocked sequential circuits
- ◆ Most commonly used
- ◆ No instability problems


⦿ Asynchronous

- ◆ Behavior depends on the *value* and *change order* of input signals at *any* instant of time
- ◆ Can be viewed as combinational circuit with feedback
- ◆ May be unstable at times

Synchronous Sequential Circuits

- Synchronization usually is achieved by a timing device: **clock generator**
 - ◆ Define the **discrete instants** of time
- Clock generator generates a periodic train of clock pulses distributed throughout the system to trigger the storage elements (flip-flops)

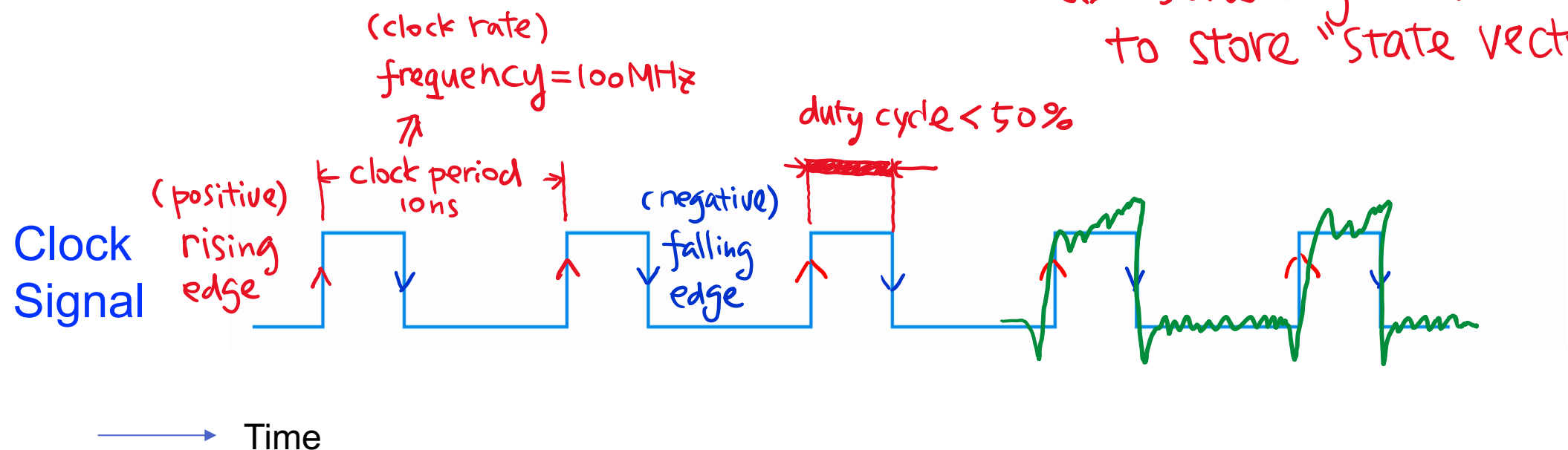as state registers
to store "state vector"



Sequential Assignment (1/4)

- The sensitivity list with edge-triggered condition


// positive edge-triggered DFF

```
reg [1:0] d, q;
```

```
always @(posedge clk) begin
```

```
    q <= d;
```

```
end
```

 


// negative edge-triggered DFF

```
reg [1:0] d, q;
```



```
always @(negedge clk) begin
```

```
    q <= d;
```

```
end
```

 

Zero-Delay Model

  

Sequential Assignment (2/4)

```
always @(posedge clk) begin  
    c = b;  
    b = a;  
end
```

Blocking assignment




- Blocking assignments are evaluated serially within a block:

```
always @(posedge clk) begin
```

```
    b = a;  
    c = b;  
end
```

race
condition

end

   

Sequential Assignment (3/4)

⦿ Non-blocking assignment



- ◆ Non-blocking assignments are evaluated in parallel within a block (hardware behavior)

```
always @(posedge clk) begin
```

```
    b <= a;
```

```
    c <= b;
```

```
end
```

 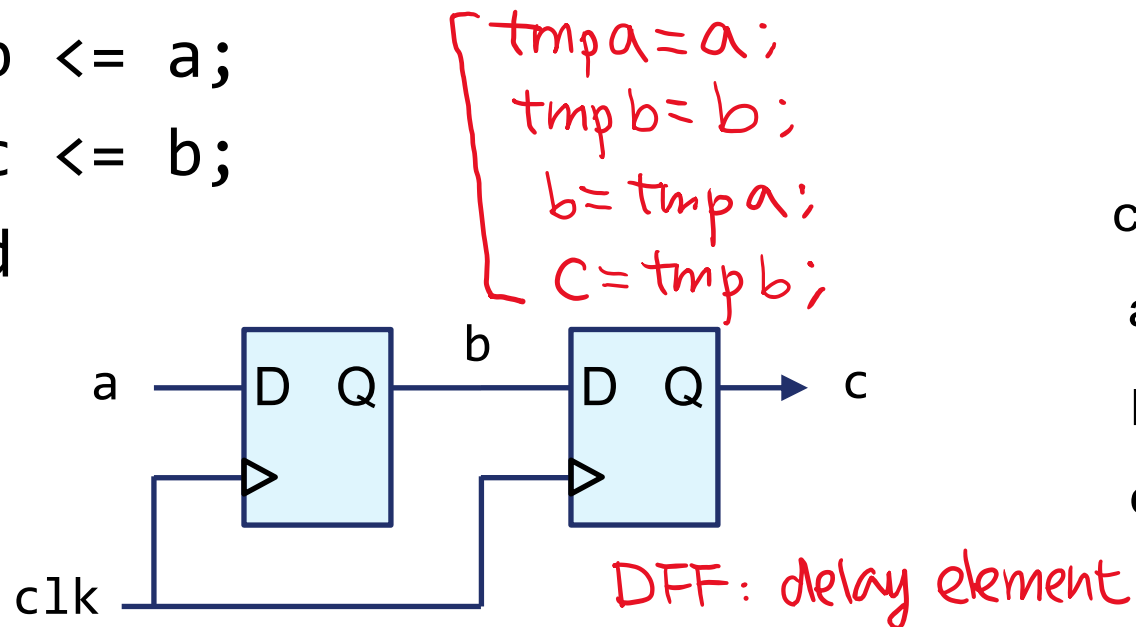


Sequential Assignment (4/4)

- Flip-flop (register) with **synchronous positive** reset

```
always @(posedge clk) begin
    if (reset) q <= 0
    else q <= d
end
```
- Flip-flop (register) with **asynchronous negative** reset

```
always @(posedge clk, negedge rst_n) begin
    if (!rst_n) q <= 0
    else q <= d
end
```
- Latch
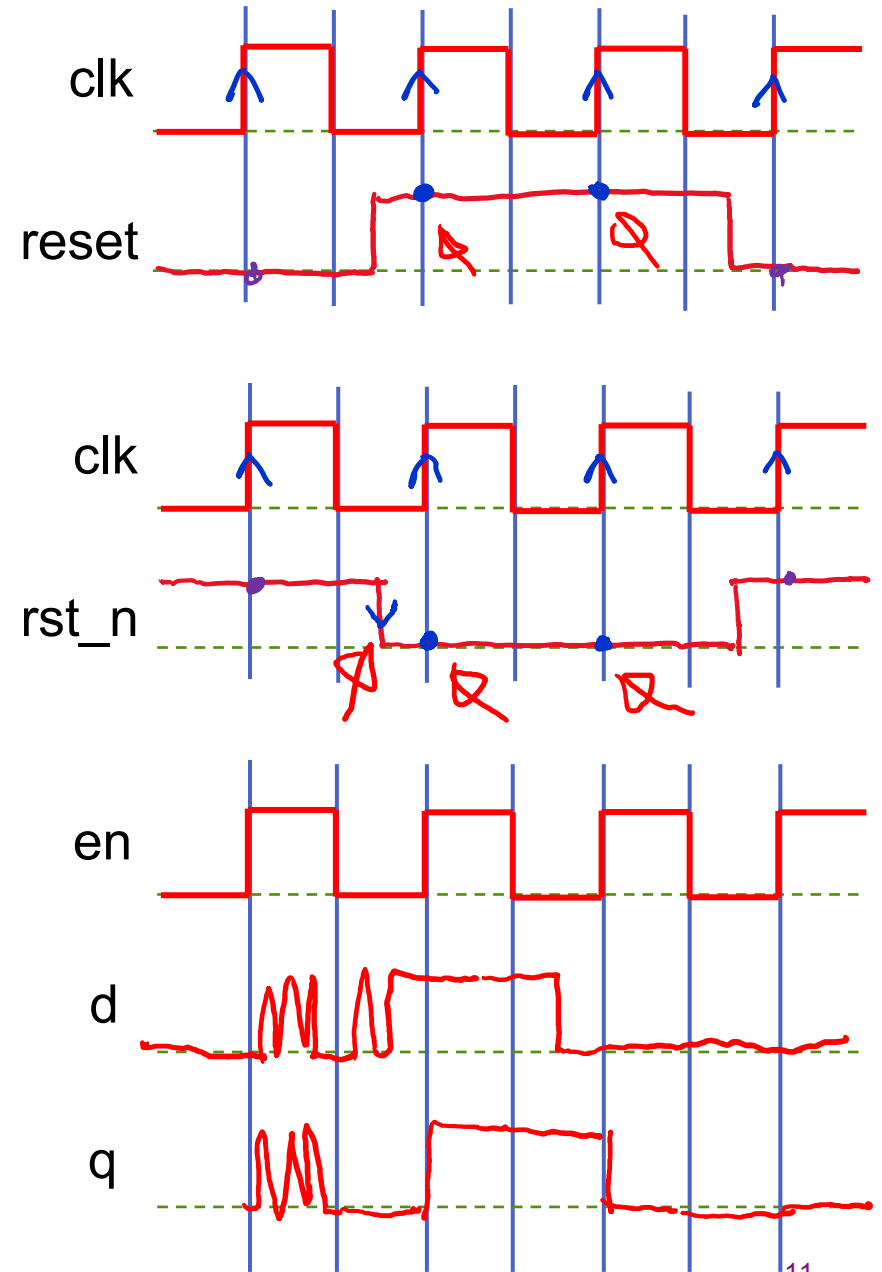
```
always @(d or en) begin
    if (en) q = d;
end
```



D Flip-Flop with Synchronous Set and Reset


```
module flipflop (q, data_in, clk, set, rst_n);  
    input      data_in, clk, set, rst_n;  
    output     q;  
    reg        q;  
  
    always @ (posedge clk) begin  
        if (rst_n == 1'b0)  
            q <= 0;  
        else if (set == 1'b1)  
            q <= 1;  
        else  
            q <= data_in;  
    end  
endmodule
```

D Flip-Flop with Asynchronous Set and Reset

```
module flipflop (q, data_in, clk, set_n, rst);  
    input  data_in, clk, set_n, rst;  
    output q;  
    reg    q;  
    always @ (posedge clk, posedge rst, negedge set_n)  
        begin  
            if (rst == 1'b1)  
                q <= 0;  
            else if (set_n == 1'b0)  
                q <= 1;  
            else  
                q <= data_in;  
        end  
endmodule
```

Register with Enable (or Load) and Asynchronous Negative Reset
 
```
reg [7:0] q;  
always @(posedge clk, negedge rst_n) begin  
    if (rst_n == 1'b0) begin  
        q <= 0;  
    end else if (en == 1'b1) begin  
        q <= d;  
    end  
end
```



Sequential Example: 4-bit Sequential Counter

4-bit Counter (1/3)

- Case 1 (putting all together) (counter1.v)

```
module counter (cnt, clk, rst_n);  
    output [3:0] cnt;  
    input clk, rst_n;  
    reg [3:0] cnt;  
    always @(posedge clk or negedge rst_n) begin  
        if (rst_n == 1'b0) begin  
            cnt <= 0;  
        end else if (cnt == 4'b1111) begin  
            cnt <= 0;  
        end else begin  
            cnt <= cnt + 1'b1;  
        end  
    end  
endmodule
```

cnt

0000
0001
0010
⋮
1110
1111
0000



boundary
condition

4-bit Counter (2/3)

- Case 2 (separate combinational and sequential parts) (counter2.v)

```
module counter (cnt, clk, rst_n);
```

```
    output [3:0] cnt;
```

```
    input  clk, rst_n;
```

```
    reg    [3:0] cnt;
```

```
    wire   [3:0] cnt_next;
```

```
    assign cnt_next = (cnt == 4'b1111) ? 0 : cnt + 1'b1;
```

```
    always @(posedge clk or negedge rst_n) begin
```

```
        if (rst_n == 1'b0) begin
```

```
            cnt <= 0;
```


```
        end else begin
```

```
            cnt <= cnt_next;
```

```
        end
```

```
    end
```

```
endmodule
```

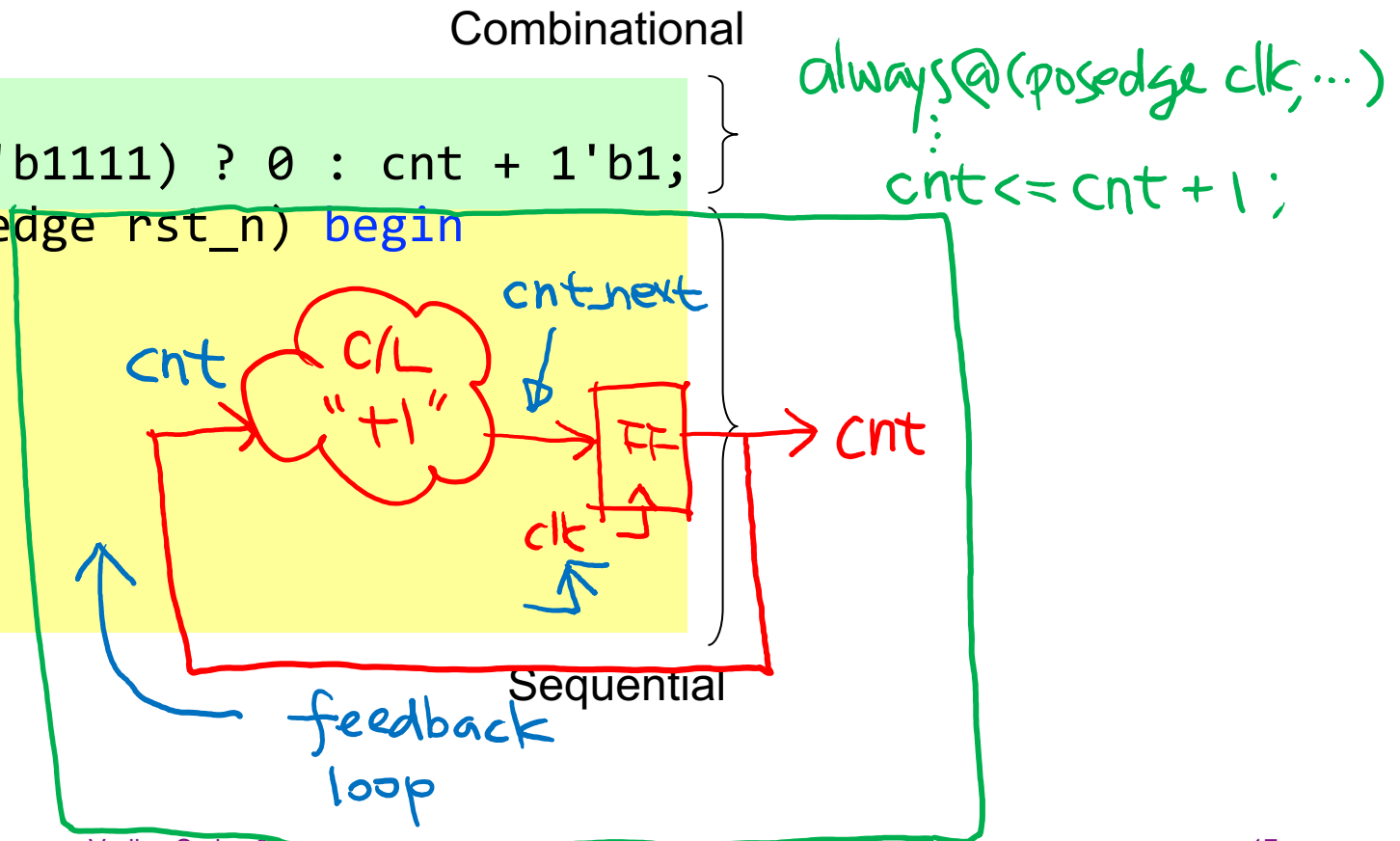


4-bit Counter (3/3)

- Case 3 (the alternative combinational description)
(counter3.v)

```
reg [3:0] cnt_next;  
always @(*) begin  
    if (cnt == 4'b1111) begin  
        cnt_next = 0;  
    end else begin  
        cnt_next = cnt + 1'b1;  
    end  
end
```

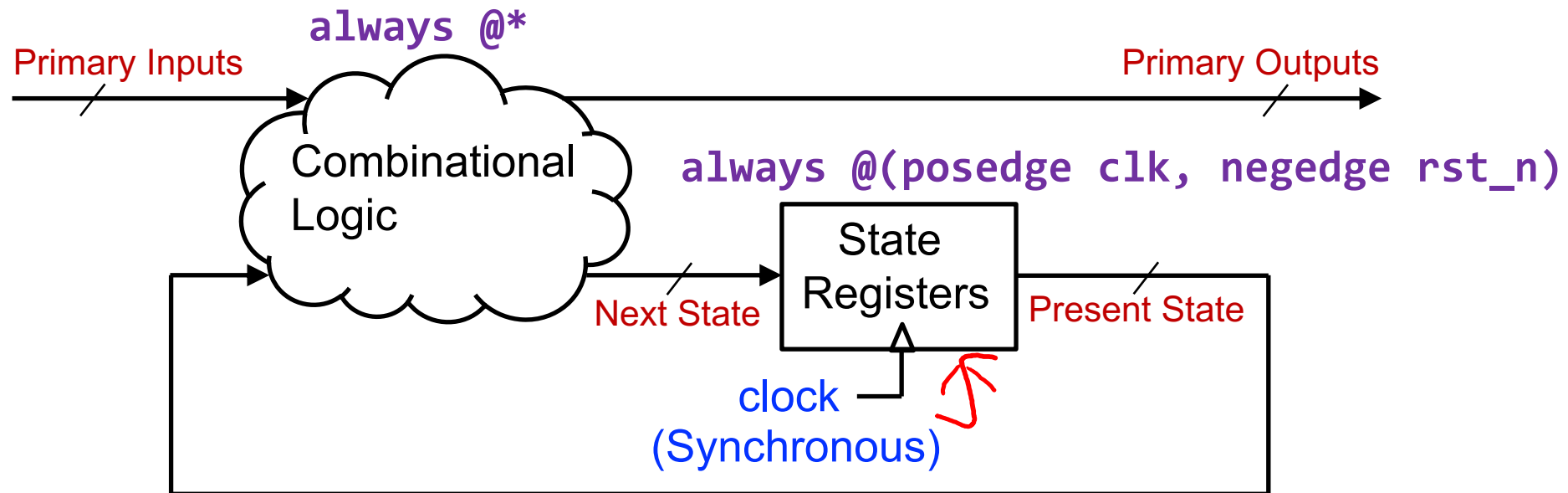★ Clocked Synchronous Sequential Circuits



Stimulus (Testbench)

◉ Example (counter_test.v)

```
`timescale 1ns/100ps
module stimulus;
  reg  clk, rst_n;
  wire [3:0] cnt;
  counter CNT1(cnt, clk, rst_n);
  always #10 clk = ~clk;
  always @(posedge clk) $display("time=%d cnt=%b", $time, cnt);
  initial begin
    clk = 0;
    rst_n = 1;
    #2  rst_n = 0;
    #20 rst_n = 1;
    #400;
    $finish;
  end
endmodule
```

initial \$monitor(\$time, "cnt=%b", cnt);

For graphical waveform

```
initial begin
  $fsdbDumpfile("stimulus.fsdb");
  $fsdbDumpvars;
end
```

Simulation Related Tasks

- ◉ To terminate simulation at a specific time


- ◆ `$finish;`

- ◉ Text-based output

- ◆ `$display`

- `always @(posedge clk)`

 - `$display("time=%d clk=%b cnt=%d", $time, clk, cnt);`



- ◆ `$monitor`

- `initial`

- `$monitor($time, " clk=%b cnt=%d", clk, cnt);`

- ◆ What's the difference?

Summary

Verilog Overview



○ Part 1

- ◆ Background
- ◆ Digital Switches and Logic Gates
- ◆ Tri-state Gates
- ◆ Structural Modeling
- ◆ Delay Model

○ Part 2

- ◆ Numbers
- ◆ Data Types
- ◆ Operators
- ◆ Compiler Directives
- ◆ Dataflow Modeling

○ Part 3

- ◆ Behavioral Modeling
- ◆ Procedural Timing Controls
- ◆ Review of Basic Module Structure
- ◆ Test Stimulus
- ◆ Tasks and Functions



○ Part 4

- ◆ Combinational Blocks
- ◆ Combinational Examples
- ◆ Module Instantiation
- ◆ Hierarchical Design Style

○ Part 5

- ◆ Sequential Blocks
- ◆ Sequential Example:
4-bit Sequential Counter

Summary for Verilog HDL Modeling

- ◉ Design with **block diagrams** before the Verilog coding
- ◉ Verilog coding philosophy is not the same as C programming
- ◉ Every Verilog RTL construct has its own logic mapping (for synthesis)
 - ◆ Combinational blocks:
 - ▣ `assign`
 - ▣ `always @*`
 - ◆ Sequential blocks:
 - ▣ `always @(posedge clk)`
- ◉ We compose **synthesizable Verilog RTL code** for digital designs
- ◉ We compose **testbenches** to verify the designs
 - ◆ Testbenches are non-synthesizable