



CT Verilog Series

Verilog Overview Part 1

Structural Modeling

黃稚存

Chih-Tsun Huang

cthuang@cs.nthu.edu.tw



國立清華大學
資訊工程學系

聲明

- ◎ 本課程之內容 (包括但不限於教材、影片、圖片、檔案資料等)，僅供修課學生個人合理使用，非經授課教師同意，不得以任何形式轉載、重製、散布、公開播送、出版或發行本影片內容 (例如將課程內容放置公開平台上，如 Facebook, Instagram, YouTube, Twitter, Google Drive, Dropbox 等等)。如有侵權行為，需自負法律責任。

Outline

- ⦿ Background
- ⦿ Digital Switches and Logic Gates
- ⦿ Tri-state Gates
- ⦿ Structural Modeling
- ⦿ Delay Model

Background

Major Hardware Description Languages (HDLs)

Interpreted Language

Object Oriented

◉ Verilog

Script

- ◆ Started by Gateway in 1983
- ◆ Became open to public by Cadence in 1990
- ◆ IEEE standard 1364 in 1995/2001/2005
- ◆ Slightly better at gate/transistor level
- ◆ Language style close to C/C++
- ◆ Pre-defined data type, easy to use

◉ VHDL

- ◆ Started by VHSIC project in 1980s
- ◆ IEEE standard 1076 in 1987, IEEE 1164 in 1993
- ◆ Slightly better at system level
- ◆ Language style close to Ada/Pascal
- ◆ User-defined data type, more flexible

Equally effective, personal preference

Design Entry


- ◉ Schematic entry (gate-level entry)
 - ◆ Or called **structural modeling**
 - ◆ Starting with structural details of a design
- ◉ HDL (RTL) entry
 - ◆ Or *behavioral entry*
 - ◆ Describing a design by structure level, **register transfer level** (RTL), behavior level or a mixture
 - ▣ **Dataflow modeling**
 - ▣ **Behavioral modeling**
- ◉ **We choose Verilog Hardware Description Language (HDL)**

Language Conventions for Verilog

- Case sensitive
- Instance of a `module` must be named
- Keywords are lower-case
- Identifiers:
 - ◆ May use upper- and lower-case alphabetical characters (`a-zA-Z`), decimal digits (`0-9`), underscore (`_`), and dollar sign (`$`)
 - ◆ May contain up to 1024 characters, and the first character must not be a digit or `$`
- Single-line comments start with “`//`”, and blocked (multi-line) comments begin with “`/*`” and end with “`*/`”
- Compiler directives begin with grave accent ``` (e.g., ``define state0 3'b001`)
- All names beginning with `$` denote **built-in system tasks** or **functions** (e.g., `$display`)

Four Logic Values in Verilog Simulation

- ◉ **0**: Logic zero, false, ground (GND)
- ◉ **1**: Logic one, true, supply voltage (Vdd, Vss)
- ◉ **X**: Unknown logic value *≠ don't care*
 - ◆ When we are not sure if it is 0 or 1
- ◉ **Z**: High impedance (high-z), floating state
- ◉ **X and Z are not practical logic values**
 - ◆ Assignment of Z to synthesize tri-state buffers by CAD tool
 - ◆ Assignment of X to propagate errors
 - ▣ Pessimistic in Verilog simulation

 

Digital Switches and Logic Gates


Logic Gates

● NAND

$$F = \overline{A \cdot B}$$


complement

and

 

● Inverter (NOT, INV)

$$F = \bar{A}$$

 


● AND

$$F = A \cdot B$$



Metal-Oxide Semiconductor (MOS) Transistor

 - ⦿ Transistor: Transfer + Resistor
- ⦿ A three-terminal device: gate, source, drain
 - ◆ (Analog) amplifier
 - ◆ (Binary) switch






Schematic Drawing of nMOS Transistor




[Source: Prof. Jing-Jia Liou]

MOS Transistors as Switches

● nMOS transistor

   

● pMOS transistor

   


Logic Gate: Inverter (INV, NOT)

CMOS inverter

- Complementary MOS: nMOS + pMOS switches


Gate-Level Schematic

 

Truth Table


A	$F = \overline{A}$
0	1
1	0

Transistor-Level Schematic

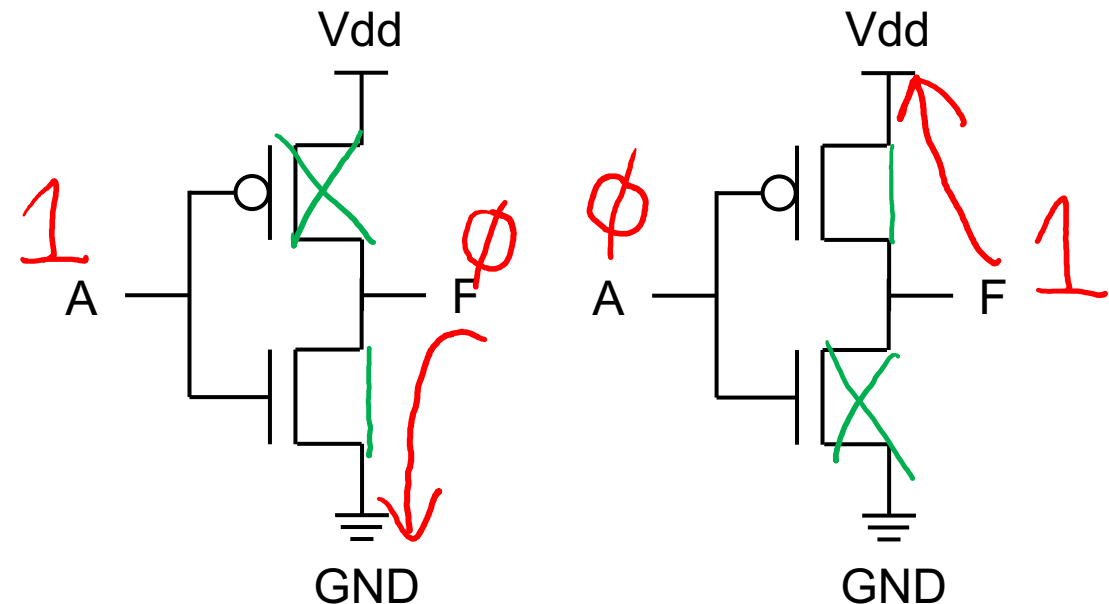

Logic Gate: NAND


Gate-Level Schematic

 


Truth Table

A	B	$F = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

Transistor-Level Schematic

 


A=1, B=1 → F=0

 

A=0, B=1 → F=1

Logic Gate: AND


Gate-Level Schematic

 

Truth Table

A	B	$F = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1


Transistor-Level Schematic

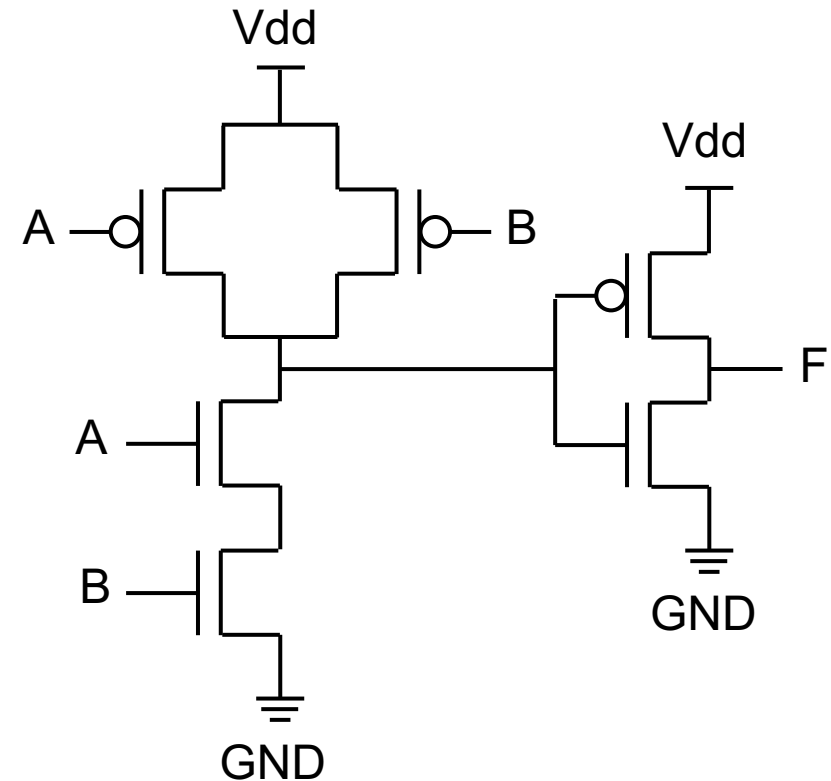

← NAND → ← NOT →

How about NOR Gate?



Gate-Level Schematic

 

Truth Table

<i>A</i>	<i>B</i>	$F = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0



Transistor-Level Schematic

  

Tri-state Gates

» Or three-state gate

Tri-State Inverter

 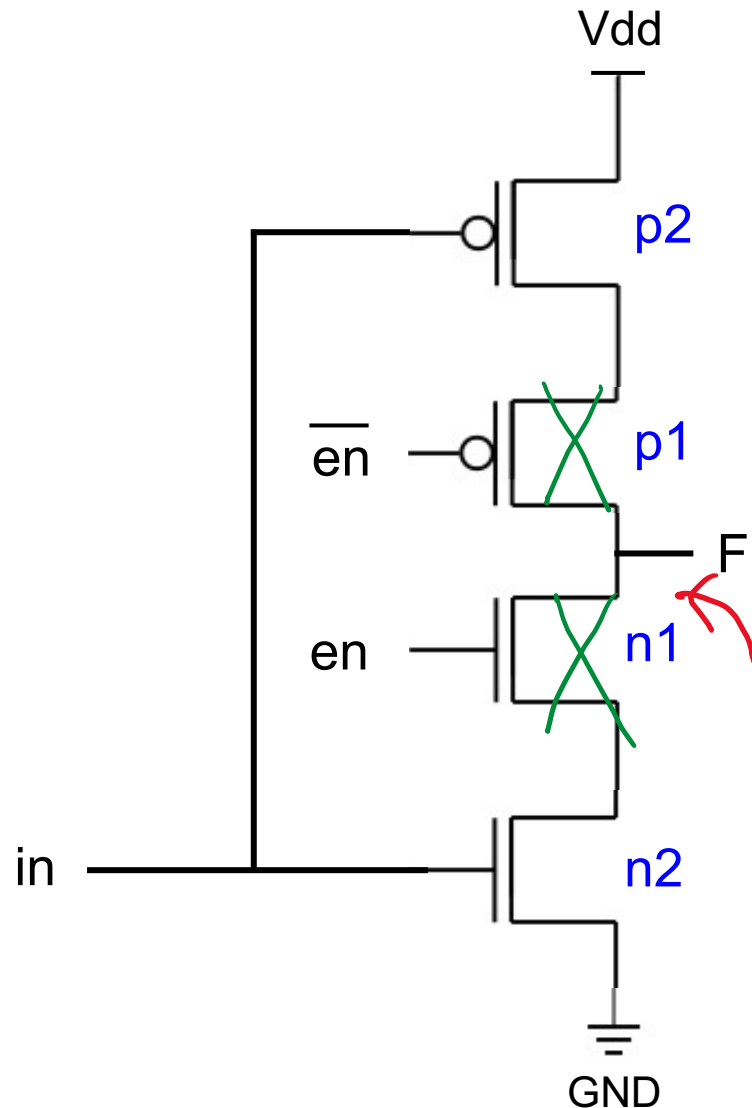

<i>en</i>	<i>F</i>
0	Z
1	<i>in</i>

① $en = 1 \rightarrow n1 \text{ on, } p1 \text{ on}$


$F = \overline{in}$

② $en = 0 \rightarrow n1 \text{ off, } p1 \text{ off}$

$F \rightarrow \text{high } Z \text{ (hi-Z)}$


or high impedance

Tri-state Buffer

 


- Output states: 0, 1, and Z (high-impedance, high-Z, or open circuits)

Tri-state Buffer


 


<i>en</i>	<i>F</i>
0	Z
1	\overline{in}

 

- Tri-state gates can be used to constructed **multiplexer**
- Tri-state gates can be used to build up a **bus**
 - ◆ A communication channel among different modules in a digital system
- Tri-state gates are not preferred inside local designs

Multiplexer with Tri-state Gates

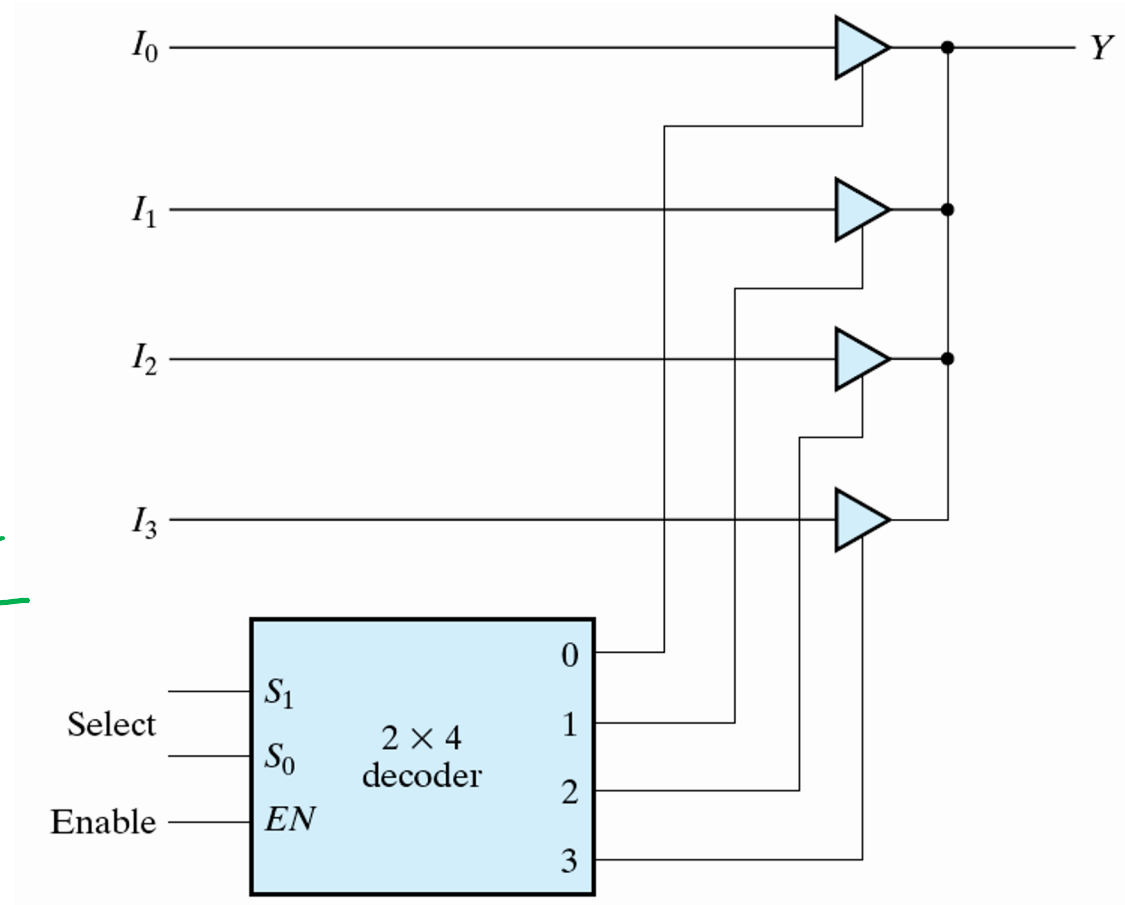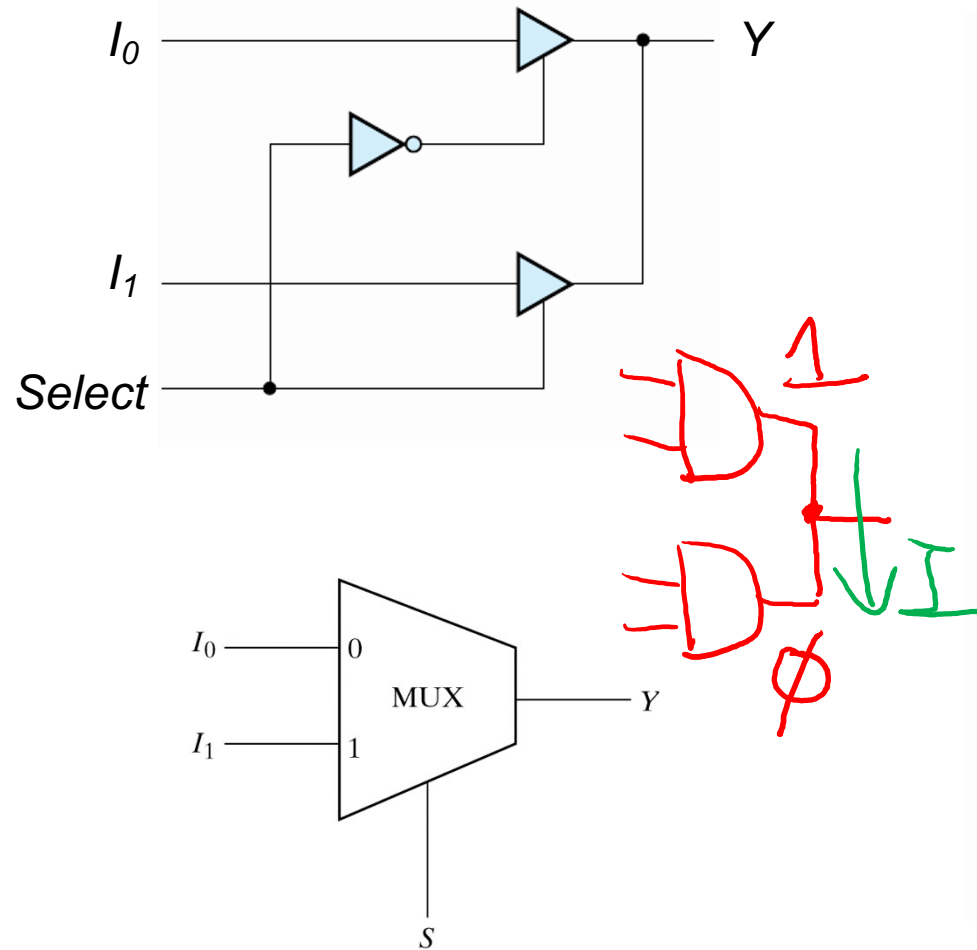


Structural Modeling

- » Or gate-level modeling

Block Diagram and Schematic



Block Diagram

 

Logic Diagram
(Gate-level Design)

Verilog Structural Description

```
module half_adder (sum, c_out, a, b);  
  input  a,b;  
  output sum, c_out;  
  wire  c_out_bar;  
  
  xor (sum, a, b);  
  nand (c_out_bar, a, b);  
  not (c_out, c_out_bar);  
endmodule
```

Module Name

Module Ports


Declaration of Port Directions

Declaration of Internal Signal

Instantiation of Primitive Gates

Output

Inputs

 

Note: All bold-faced items are Verilog keywords.

Verilog Predefined Primitives (1/2)

- ◉ Single-input gates

- ◆ buf, not

- ◉ Multi-input gates

- ◆ and, nand, or, nor, xor, xnor

- ◉ Tri-state gates

- ◆ bufif0, bufif1, notif0, notif1

Verilog Predefined Primitives (2/2)

- ⦿ Never used stand-alone in a design, must be instantiated within a module
- ⦿ Identifier (instance name) is optional
- ⦿ Default delay = 0
 - ◆ Zero-delay model
- ⦿ Port elements of an instantiated primitive must be output followed by inputs
 - ◆ The number of inputs can vary
- ⦿ Verilog also supports User-Defined Primitive (UDP)

Optional Primitive Identifiers

```
module half_adder (sum, c_out, a, b);  
    input    a, b;  
    output   sum, c_out;  
    wire     c_out_bar;
```

Reference


Instance Name

```
    xor g1 (sum, a, b);  
    nand (c_out_bar, a, b);  
    not g2 (c_out, c_out_bar);  
endmodule
```

c_out_bar

g1, g2 are primitive identifiers.

 An undeclared variable is assumed to be a single-bit wire.



Truth Tables of Primitive Gates

- For Verilog **simulation**

and	0	1	x	z	nor	0	1	x	z	xor	0	1	x	z	in	buf
0	0	0	0	0	0	1	0	x	x	0	0	1	x	x	0	0
1	0	1	x	x	1	0	0	0	0	1	1	0	x	x	1	1
0/1 x	0	0/1 x	x	x	x	x	0	x	x	x	x	x	x	x	x	x
z	0	x	x	x	z	x	0	x	x	z	x	x	x	x	z	x

nand	0	1	x	z	or	0	1	x	z	xnor	0	1	x	z	in	not
0	1	1	1	1	0	0	1	x	x	0	1	0	x	x	0	1
1	1	0	x	x	1	1	1	1	1	1	0	1	x	x	1	0
x	1	x	x	x	x	x	1	x	x	x	x	x	x	x	x	x
z	1	x	x	x	z	x	1	x	x	z	x	x	x	x	z	x


Four-Value Simulation for Binary System

- ⦿ 0: Logic zero, false
- ⦿ 1: Logic one, true
- ⦿ z: High impedance, floating state
- ⦿ x: Unknown logic value for pessimistic simulation

◆ $x \& 0 =$ _____	$z \mid 0 =$ _____
◆ $x \& 1 =$ _____	$z \mid 1 =$ _____
◆ $x \wedge 1 =$ _____	$x \& z =$ _____
◆ $z \wedge 1 =$ _____	$z \& z =$ _____
◆ $\sim x =$ _____	$\sim z =$ _____

Gate-Level Multiplexer (1/3)


Block Diagram

 

Truth Table

s1	s0	out
0	0	i0
0	1	i1
1	0	i2
1	1	i3

Logic Diagram

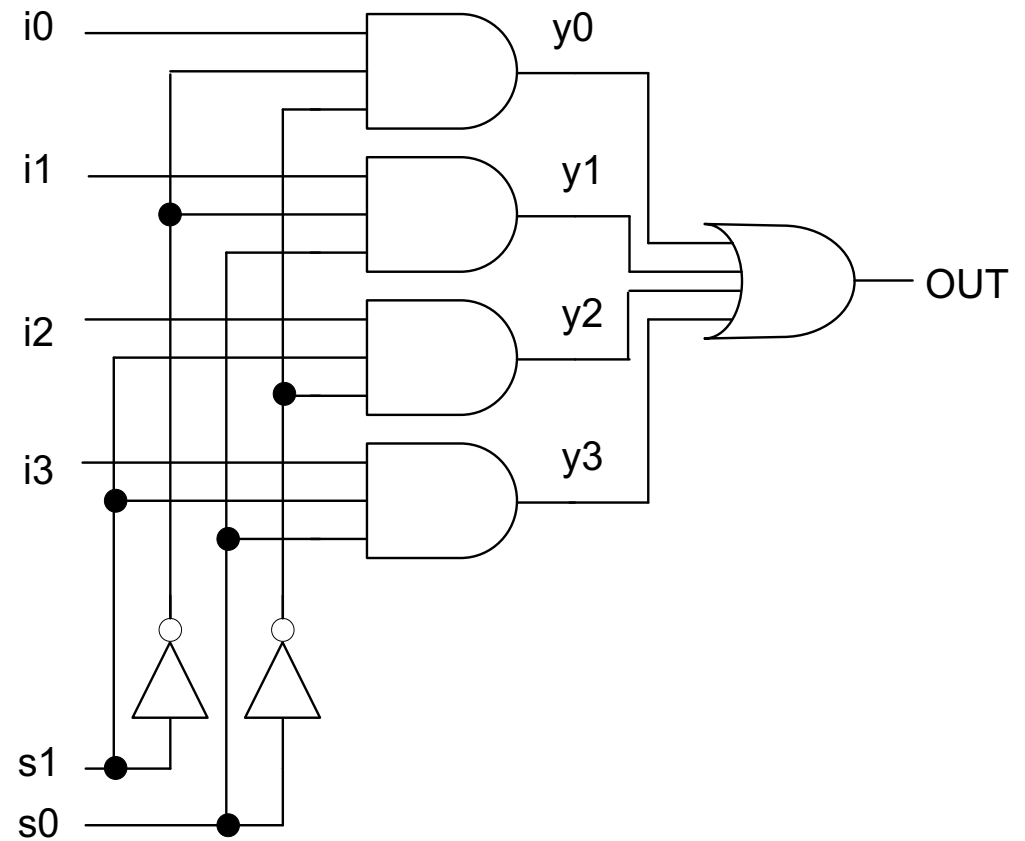

Gate-Level Multiplexer (2/3)

```
module mux4_to_1 (out, i0, i1, i2, i3, s1, s0);  
    output out;  
    input i0, i1, i2, i3;  
    input s1, s0;  
    wire s1n, s0n;  
    wire y0, y1, y2, y3;  
    not (s1n, s1);  
    not (s0n, s0);  
    and (y0, i0, s1n, s0n);  
    and (y1, i1, s1n, s0);  
    and (y2, i2, s1, s0n);  
    and (y3, i3, s1, s0);  
    or (out, y0, y1, y2, y3);  
endmodule
```

- ⦿ Instance names are optional for Verilog primitives
 - ◆ Mandatory for user-defined modules


Gate-Level Multiplexer (3/3)

```
`timescale 1ns/100ps
module stimulus;
  reg IN0, IN1, IN2, IN3;
  reg S1, S0;
  wire OUT;
  mux4_to_1 mymux(OUT, IN0, IN1, IN2, IN3, S1, S0);
  initial begin
    IN0 = 1; IN1 = 0; IN2 = 1; IN3 = 0;
    #1 S1 = 0; S0 = 0;
    #1 S1 = 0; S0 = 1;
    #1 S1 = 1; S0 = 0;
    #1 S1 = 1; S0 = 1;
  end
  initial
    $monitor($time,
      " {IN3, IN2, IN1, IN0} = %b, {S1, S0} = %b, OUT = %b",
      {IN3, IN2, IN1, IN0}, {S1, S0}, OUT);
endmodule
```

Delay Model

Basic Delay Model

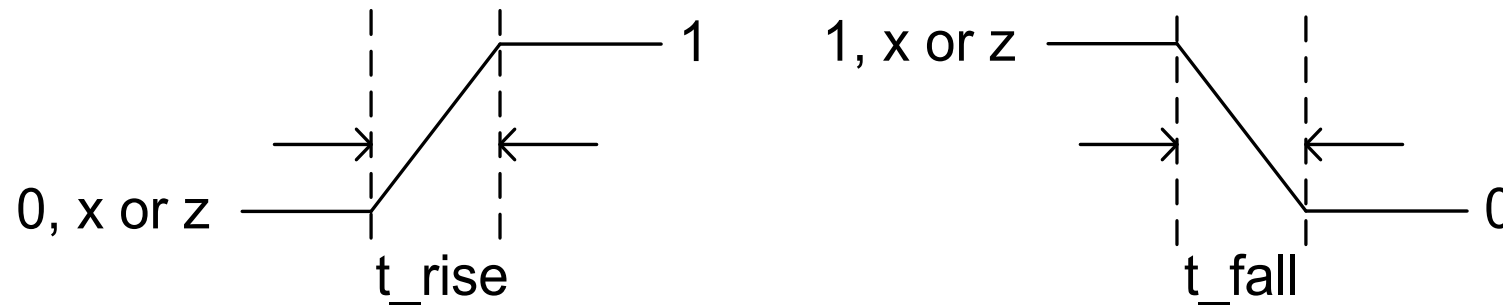- ⦿ Rise delay: rising edge (or positive edge): 0, x, or z \rightarrow 1
- ⦿ Fall delay: falling edge (or negative edge): 1, x, or z \rightarrow 0



- ⦿ Turn-off delay
 - ◆ The delay associated with a gate output transition to the high z from another value
 - $0 \rightarrow z$
 - $1 \rightarrow z$
- ⦿ When the value changes to x
 - ◆ $\min\{\text{rise delay, fall delay, turn-off delay}\}$

Gate Delay (1/2)

```
bufif0 #(rise_del, fall_del, turnoff_del) b1(out, in, ctrl);
```

```
and #(rise_del, fall_del) a2(out, i1, i2);
```

- If 2 delays specified, e.g., `#(delay1, delay2)`

- ◆ `#(delay1, delay2, min(delay1, delay2))`

```
and #(rise_del) a2(out, i1, i2);
```

- If only 1 delay specified, e.g., `#(delay1)`

- ◆ `#(delay1, delay1, delay1)`

- If no delay specified

- ◆ The default value is zero (zero-delay model)


Gate Delay (2/2)

- Each delay specification can be further modeled as

- ◆ min:typical:max (minimum:typical:maximum)
and #(4:5:6) a1(out, i1, i2);
and #(3:4:5, 5:6:7) a2(out, i1, i2);
and #(2:3:4, 3:4:5, 4:5:6) a3(out, i1, i2);

- For NC Verilog simulator

 
- \$ ncverilog test.v +maxdelays
\$ ncverilog test.v +mindelays
\$ ncverilog test.v +typdelays



Critical Delay and Critical Path

- Critical delay (timing) determines the operating clock speed (frequency)
 - ◆ Improve speed -> shorten critical delay
 
```
module D (out, a, b, c);  
    output out;  
    input a, b, c;  
  
    // Internal nets  
    wire e;  
  
    and #(5) a1(e, a, b);  
    or  #(4) o1(out, e, c);  
endmodule
```



Test Stimulus Example


```
`timescale 1ns/100ps
module stimulus;
    reg A, B, C;
    wire OUT;
    D d1( OUT, A, B, C);

    initial
        $monitor($time,
            " A= %b, B=%b, C= %b, OUT= %b\n", A, B, C, OUT);

    initial begin
        #10 A= 1'b0; B= 1'b0; C= 1'b0;
        #10 A= 1'b1; B= 1'b1; C= 1'b1;
        #10 A= 1'b1; B= 1'b0; C= 1'b0;
        #20 $finish;
    end
endmodule
```

Simulation with Delay Model

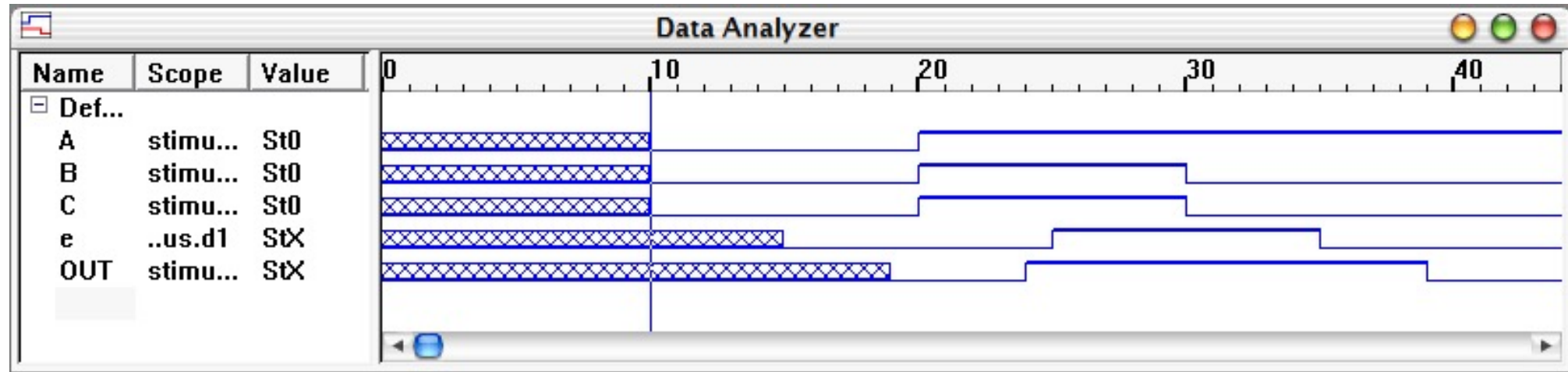- ◉ **reg**-type variable is unknown (X) initially for NC Verilog
 - ◆ Different simulators may behave differently
 - ▣ Some other simulators assume that the initial value is zero
 - ◆ Pessimistic



- ◉ How about **wire**-type variable? ∞
wire out;