

Finite-State Machines

黃稚存

Chih-Tsun Huang

cthuang@cs.nthu.edu.tw



國立清華大學
資訊工程學系

聲明

- ◎ 本課程之內容 (包括但不限於教材、影片、圖片、檔案資料等)，僅供修課學生個人合理使用，非經授課教師同意，不得以任何形式轉載、重製、散布、公開播送、出版或發行本影片內容 (例如將課程內容放置公開平台上，如 Facebook, Instagram, YouTube, Twitter, Google Drive, Dropbox 等等)。如有侵權行為，需自負法律責任。

Outline

- ◉ Mealy machine and Moore machine
- ◉ Coding Guidelines
- ◉ Example: Level-to-Pulse Converter
- ◉ Example: FSM X
- ◉ Example: Newspaper Vending Machine
- ◉ Summary

digital design




datapath + finite-state machine
(FSM)

Mealy Machine and Moore Machine


Finite State Machines

Moore machine and Mealy machine

 

Moore Outputs


Outputs depend solely on state vector

 


Mealy Outputs

Outputs depend on inputs and state vector

Moore Machine

 

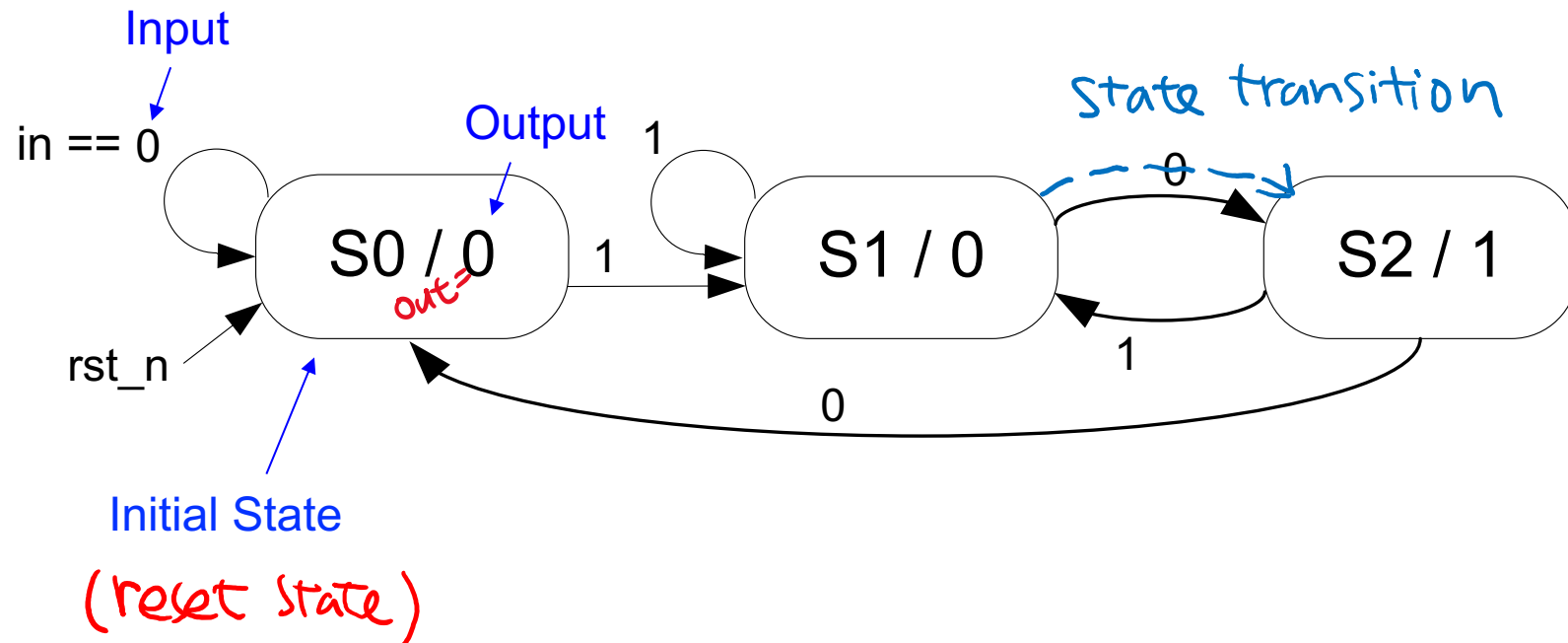- Recognizing the “10” sequence among the input bit stream



Moore Machine Coding

```
parameter S0 = 2'b00;
parameter S1 = 2'b01;
parameter S2 = 2'b10;
reg [2:0] state, next_state;
always @(posedge clock, negedge rst_n)
begin
    if (rst_n == 1'b0)
        state <= S0;
    else
        state <= next_state;
end
always @* begin
    next_state = S0;
    case (state)  $\Gamma out = \phi;$ 
        S0: begin
            if (in == 1)
                next_state = S1;
            else
            next_state = S0;
        end
    end
```

State Update
(Sequential)


```
S1: begin
    if (in == 1)
        next_state = S1;
    else
        next_state = S2;
end
S2: begin  $\langle out = 1;$ 
    if (in == 1)
        next_state = S1;
    else
    next_state = S0;
end
endcase // case end
end //always end
 $\times$  assign out = state == S2 ? 1 : 0;
```

State Transition
(Combinational)

Outputs
(Combinational)

Mealy Machine

 - Recognizing the “10” sequence among the input bit stream



Mealy Machine Coding

```

parameter S0 = 1'b0;
parameter S1 = 1'b1;
reg state, next_state;
always @(posedge clk, negedge rst_n) begin
    if (rst_n == 1'b0)
        state <= S0;
    else
        state <= next_state;
end
always @* begin
    next_state = S0;
    case(state)
        S0: begin
            if (in == 1)
                next_state = S1;
            else
                next_state = S0;
        end
    end
end

```

State Update
(Sequential)

State Transition
(Combinational)

Handwritten notes:
 - *out = 0;* (next to S0 case)
 - *begin* (above S1 assignment)
 - *end* (below S1 assignment)

```

S1: begin
    if (in == 1)
        next_state = S1;
    else
        next_state = S0;
end
endcase // case end
end // always end
assign out =
    (state == S1 && in == 0) ? 1 : 0;


```

Outputs
(Combinational)

Handwritten notes:
 - *begin* (above S1 if)
 - *out = 1;* (next to S1 if)
 - *end* (below S1 if)
 - *else* (below S1 if)
 - *next_state = S0;* (below S1 if)
 - *end* (below S1 if)
 - *endcase // case end* (below S1 if)
 - *end // always end* (below S1 if)
 - *assign out =* (above output assignment)
 - *(state == S1 && in == 0) ? 1 : 0;* (output assignment)

Coding Guidelines

FSM (Sequential Block) Modeling

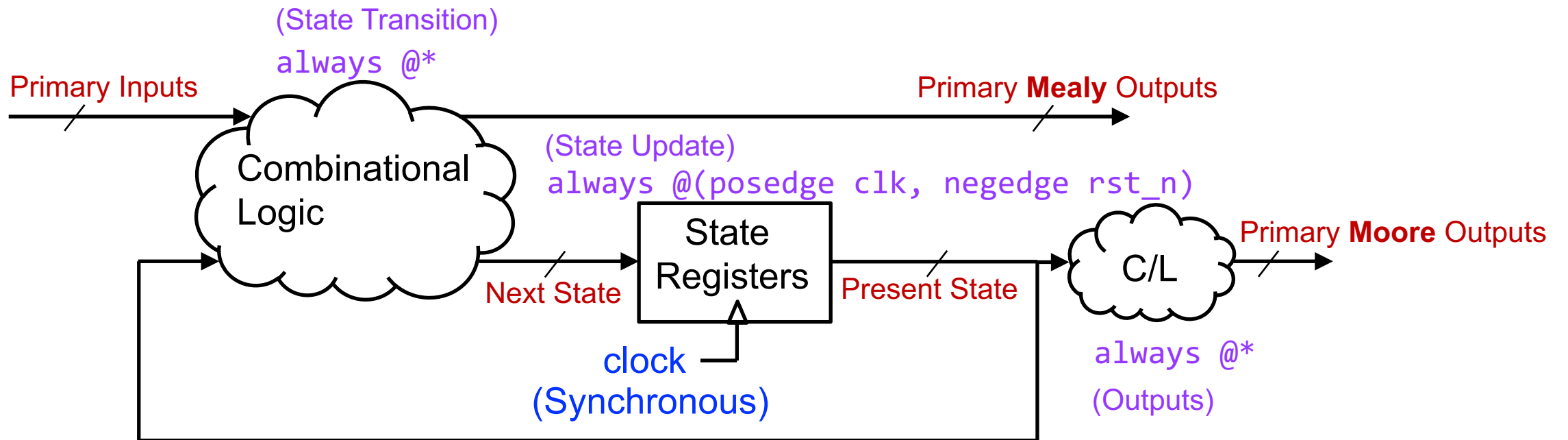

Guidelines for FSM Modeling

- ⦿ An `always` block for updating **state registers**
 - ◆ Sequential block
- ⦿ An `always` block for **state transition (next state)**
 - ◆ Combinational block
- ⦿ An optional `always` block for **output** generation
 - ◆ Combinational block
- ⦿ Parameterize all state encoding


Moore vs. Mealy (1/2)

⦿ Difference


- ◆ Moore: outputs depend on state only
- ◆ Mealy: outputs depend on state and inputs
 - ▣ Might be less straightforward
 - ▣ Generally fewer states
- ◆ Any timing difference?

Moore vs. Mealy (2/2)

Moore

 

Mealy

 

clock


Input

Moore
State

Moore
Output

Mealy
State

Mealy
Output

 

Timing Difference



Example: Level-to-Pulse Converter


Level-to-Pulse Converter

- A level-to-pulse converter
 - ◆ Produces a single-cycle pulse each time its input goes high
 - ◆ Synchronous rising-edge detector
- Applications
 - ◆ Pushbuttons and switches pressed by humans
 - ◆ Single-cycle enable signals




Finite-State Machine

Moore

 


Mealy

 

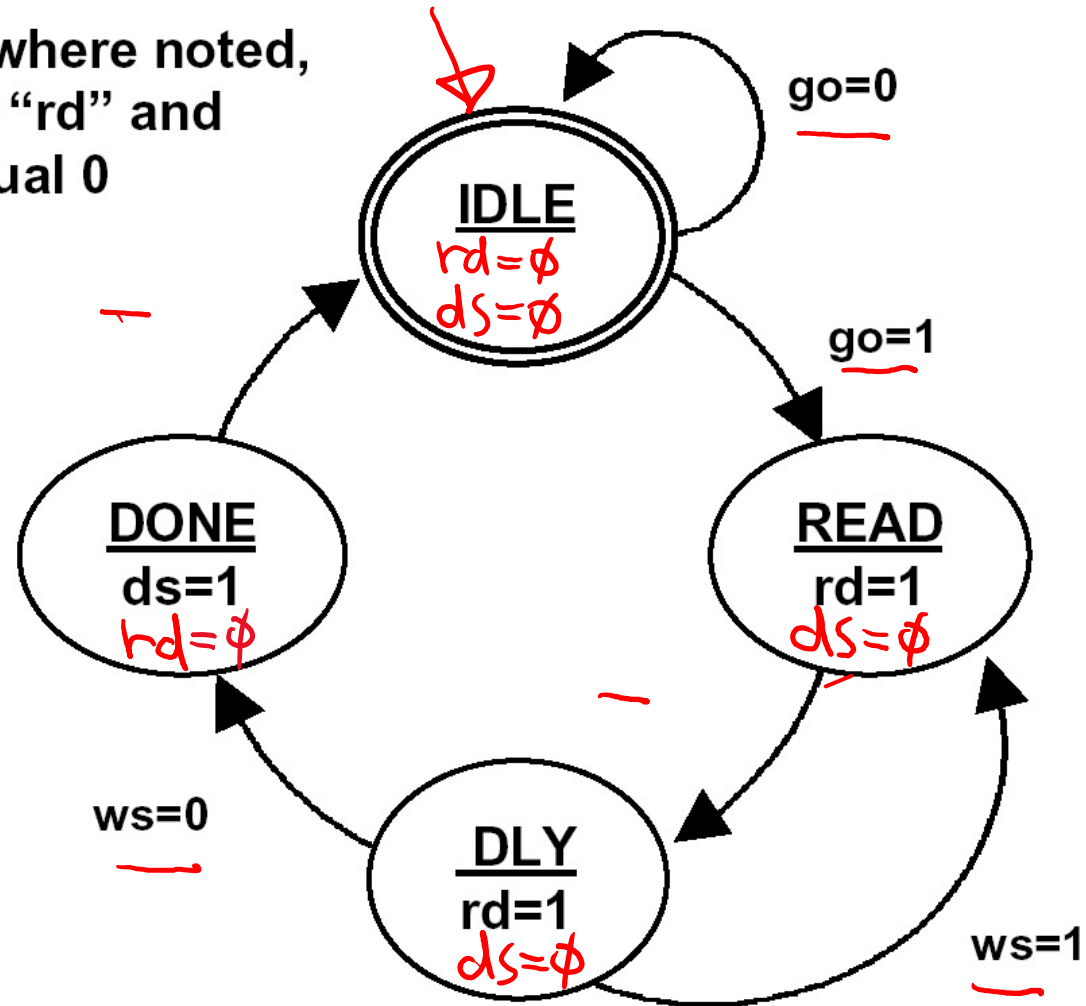Example: FSM X

FSM X

Except where noted,
outputs “rd” and
“ds” equal 0



Coding Example 1

```
module fsm1 (ds, rd, go, ws, clk, rst_n);
    output ds, rd;
    input go, ws;
    input clk, rst_n;
    parameter [1:0]
        IDLE = 2'b00,
        READ = 2'b01,
        DLY = 2'b10,
        DONE = 2'b11;
    reg [1:0] state, next;
    always @(posedge clk or negedge rst_n)
        if (!rst_n) state <= IDLE;
        else state <= next;
```

```
    always @* begin
        next = IDLE;
        case (state)
            IDLE: if (go) next = READ;
                  else next = IDLE;
            READ: next = DLY;
            DLY:  if (ws) next = READ;
                  else next = DONE;
            DONE: next = IDLE;
        endcase
    end
    assign rd = (state==READ || state==DLY);
    assign ds = (state==DONE);
endmodule
```

Coding Example 2

```
module fsm2 (ds, rd, go, ws, clk, rst_n);
    output ds, rd;
    input go, ws;
    input clk, rst_n;
    reg ds, rd;
    parameter [1:0]
        IDLE = 2'b00,
        READ = 2'b01,
        DLY = 2'b10,
        DONE = 2'b11;
    reg [1:0] state, next;
    always @(posedge clk or negedge rst_n)
        if (!rst_n) state <= IDLE;
        else state <= next;
```


```
    always @* begin
        next = IDLE;
        ds = 1'b0;
        rd = 1'b0;
        case (state)
            IDLE: if (go) next = READ;
                  else next = IDLE;
            READ: begin
                rd = 1'b1;
                next = DLY;
            end
            DLY: begin
                rd = 1'b1;
                if (ws) next = READ;
                else next = DONE;
            end
            DONE: begin
                ds = 1'b1;
                next = IDLE;
            end
        endcase
    end
endmodule
```

Coding Example 3

```
module fsm3 (ds, rd, go, ws, clk, rst_n);  
    output ds, rd;  
    input go, ws;  
    input clk, rst_n;
```

```
    parameter [2:0]  
        IDLE = 3'b0_00,  
        READ = 3'b0_01,  
        DLY = 3'b1_01,  
        DONE = 3'b0_10;
```
 
```
    reg [2:0] state, next;  
    always @(posedge clk or negedge rst_n)  
        if (!rst_n) state <= IDLE;  
        else state <= next;
```



```
    always @* begin  
        next = IDLE;  
        case (state)  
            IDLE: if (go) next = READ;  
                  else next = IDLE;  
            READ: next = DLY;  
            DLY: if (ws) next = READ;  
                  else next = DONE;  
            DONE: next = IDLE;  
        endcase  
    end
```




```
    assign {ds,rd} = state[1:0];
```

```
endmodule
```

  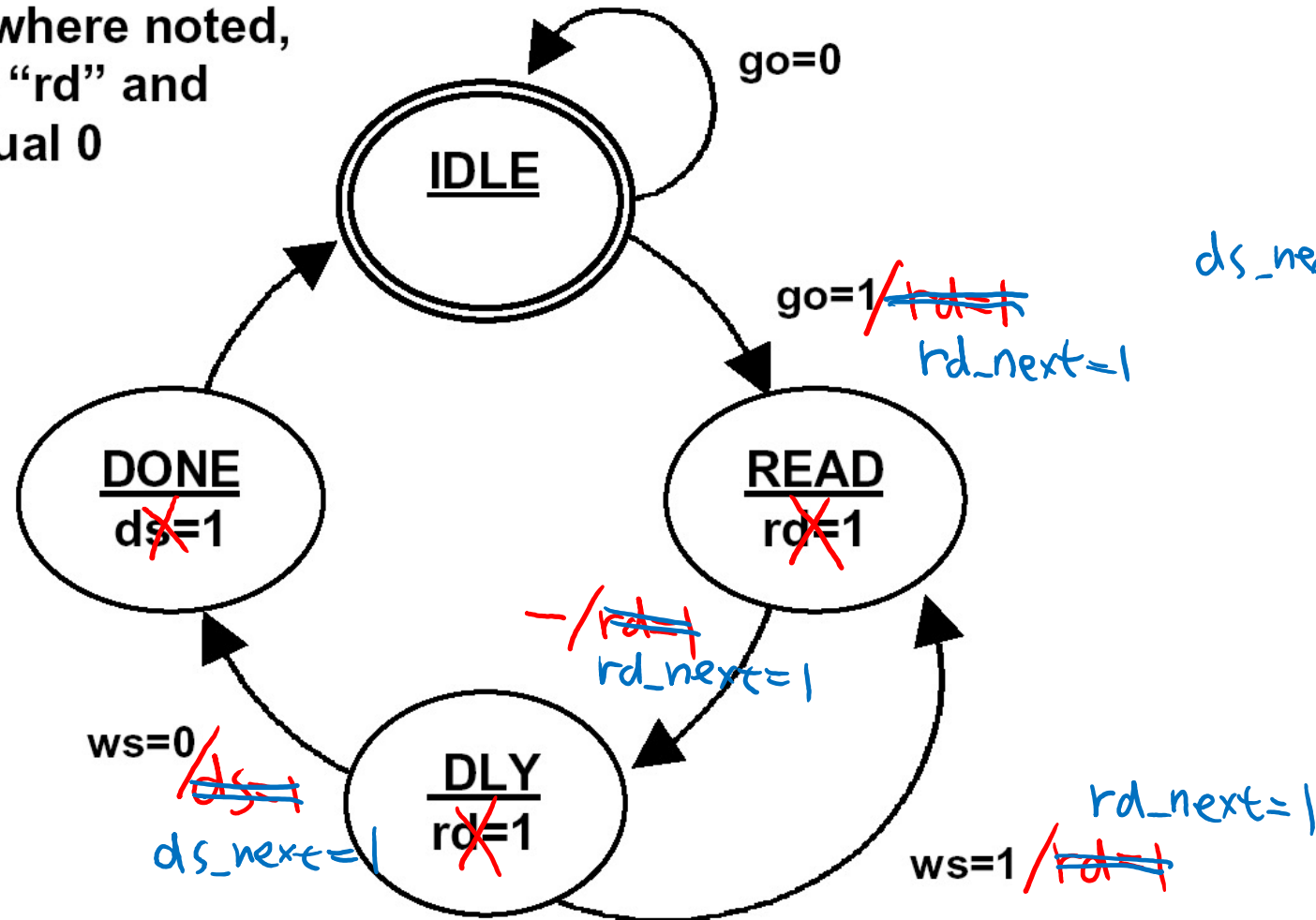Example: FSM X

Can you change it to Mealy Machine?

Except where noted,
outputs "rd" and
"ds" equal 0



Part of Stimulus for FSM X

```
initial begin
    clk = 0;
    rst_n = 1;
    go = 0;
    ws = 0;

    #(cyc/2);
    #(cyc*2) rst_n = 0;
    #(cyc*2) rst_n = 1;

    #(cyc);
    #(cyc);
    #(cyc) go = 1; ws = 1;
    #(cyc*3);
    #(cyc); ws = 0;
    #(cyc); go = 0;
    #(cyc*5);
    $finish;
end
```

Example: Newspaper Vending Machine

Newspaper Vending Machine Example


⦿ Rule:

- ◆ Each newspaper cost 15 Dollars
- ◆ Only 10 and 5 Dollars coin
- ◆ No change
- ◆ Possible combination: 3x 5 coins, one 10 coin and one 5 coin. Other combinations are not allowable.

⦿ Requirements:

- ◆ Send out control signal for each coin inserted
- ◆ One output signal which enable newspaper delivery
- ◆ One reset signal to reset the vending machine

State Diagram

 

FSM Verilog Code (1/2)

```
module vend (  
    coin, clock, reset, newspaper  
);  
    input [1:0] coin;  
    input clock;  
    input reset;  
    output newspaper;  
    reg newspaper;  
    reg [1:0] state, next_state;  
  
    // state encoding  
    parameter s0 = 2'b00;  
    parameter s5 = 2'b01;  
    parameter s10 = 2'b10;  
    parameter s15 = 2'b11;
```

```
// combinational  
always @* begin  
    case (state)  
        s0: begin  
            if (coin == 2'b10) begin  
                newspaper = 1'b0;  
                next_state = s10;  
            end else if (coin == 2'b01) begin  
                newspaper = 1'b0;  
                next_state = s5;  
            end else begin  
                newspaper = 1'b0;  
                next_state = s0;  
            end  
        end  
    end  
    s5: begin  
        if (coin == 2'b10) begin  
            newspaper = 1'b0;  
            next_state = s15;
```

FSM Verilog Code (2/2)

```
        end else if (coin == 2'b01) begin
            newspaper = 1'b0;
            next_state = s10;
        end else begin
            newspaper = 1'b0;
            next_state = s5;
        end
    end
end
s10: begin
    if (coin == 2'b10) begin
        newspaper = 1'b0;
        next_state = s15;
    end else if (coin == 2'b01) begin
        newspaper = 1'b0;
        next_state = s15;
    end else begin
        newspaper = 1'b0;
        next_state = s10;
    end
end
end
```

```
s15: begin
    newspaper = 1'b1;
    next_state = s0;
end
default: begin
    newspaper = 1'b0;
    next_state = s0;
end
endcase
end

// state update, synchronous reset
always @(posedge clock) begin
    if (reset == 1'b1)
        state = s0;
    else
        state = next_state;
    end
endmodule
```

Summary

- ◉ Design your FSM before Verilog coding
 - ◆ Define states, state transitions, and outputs clearly
- ◉ Follow the coding guidelines
 - ◆ Explicit combinational blocks (state transition / output logic) + sequential block (state registers)
- ◉ One design can have multiple FSMs
 - ◆ Keep each FSM simple enough
- ◉ One state can execute for multiple clock cycles
- ◉ **FSM must be able to return its initial state without using the reset**

