



EECS 2070 02 Fall 2021

# Digilent Basys3 FPGA Board Part 2

黃稚存

Chih-Tsun Huang

[cthuang@cs.nthu.edu.tw](mailto:cthuang@cs.nthu.edu.tw)



國立清華大學  
資訊工程學系

Lecture 07

# 聲明

- ◎ 本課程之內容 (包括但不限於教材、影片、圖片、檔案資料等)，僅供修課學生個人合理使用，非經授課教師同意，不得以任何形式轉載、重製、散布、公開播送、出版或發行本影片內容 (例如將課程內容放置公開平台上，如 Facebook, Instagram, YouTube, Twitter, Google Drive, Dropbox 等等)。如有侵權行為，需自負法律責任。

# Outline


- ① Seven-Segment Display
- ① Pushbuttons & Debounce Circuit
- ① One-Pulse Generator
- ① Summary

→ Reference: Digilent Basys3™ FPGA Board Reference Manual



# Seven-Segment Display
 
# Seven Segment


- ④ Four-digit common anode (共陽) seven-segment LED display
- ④ 128 possible patterns on a digit
  - ◆ Ten decimal patterns are the most useful




Source: Wikipedia

  


# Decimal Number Code

 

# Common Anode Circuit Node

 


# IO Mapping and Interface

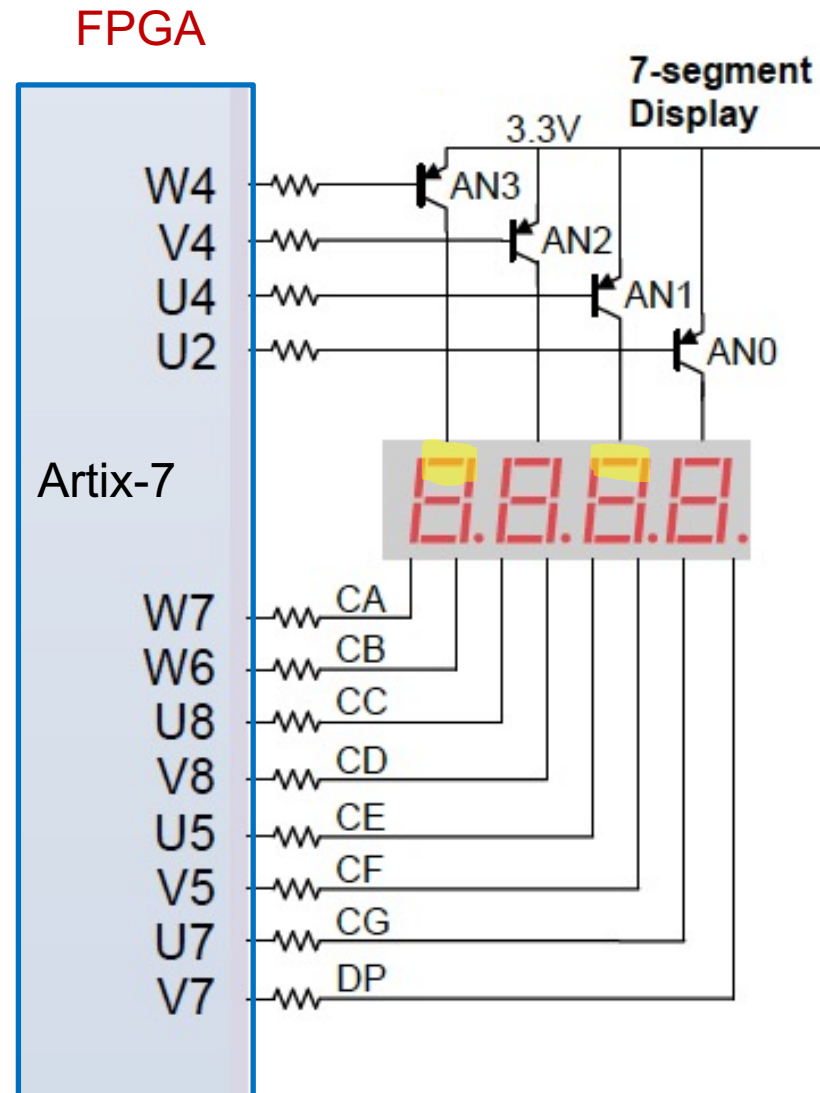


 
# Control of Seven-Segment Display (1/5)


- ⦿ The cathodes of similar segments on all four displays are connected to the same FPGA pins



symbol	A	B	C	D	E	F	G
FPGA pin	W7	W6	U8	V8	U5	V5	U7

 
# Control of Seven-Segment Display (2/5)

- 7 pins to control each 7-segment display
- 4 pins to choose which 7-segment to display
- Each device is negative enabled (low enabled)



 
# Control of Seven-Segment Display (3/5)

- Input:  $\{AN3\ AN2\ AN1\ AN0\}$   
 $D_3\ D_2\ D_1\ D_0 = 1110$   
 $A\ B\ C\ D\ E\ F\ G = 0000001$
- What is the response?


 
# Control of Seven-Segment Display (4/5)


- Input:  $\{AN3\ AN2\ AN1\ AN0\}$   
 $D_3\ D_2\ D_1\ D_0 = 1110$   
 $A\ B\ C\ D\ E\ F\ G = 0000001$
- What is the response?



# Control of Seven-Segment Display (5/5)


- Question: How to display four different numbers (e.g., **1234**)?
- Solution: **Time multiplexing**

	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
Display '4':	1	0	0	1
Display '3':	0	0	0	1
Display '2':	0	0	1	0
Display '1':	1	0	0	1

 
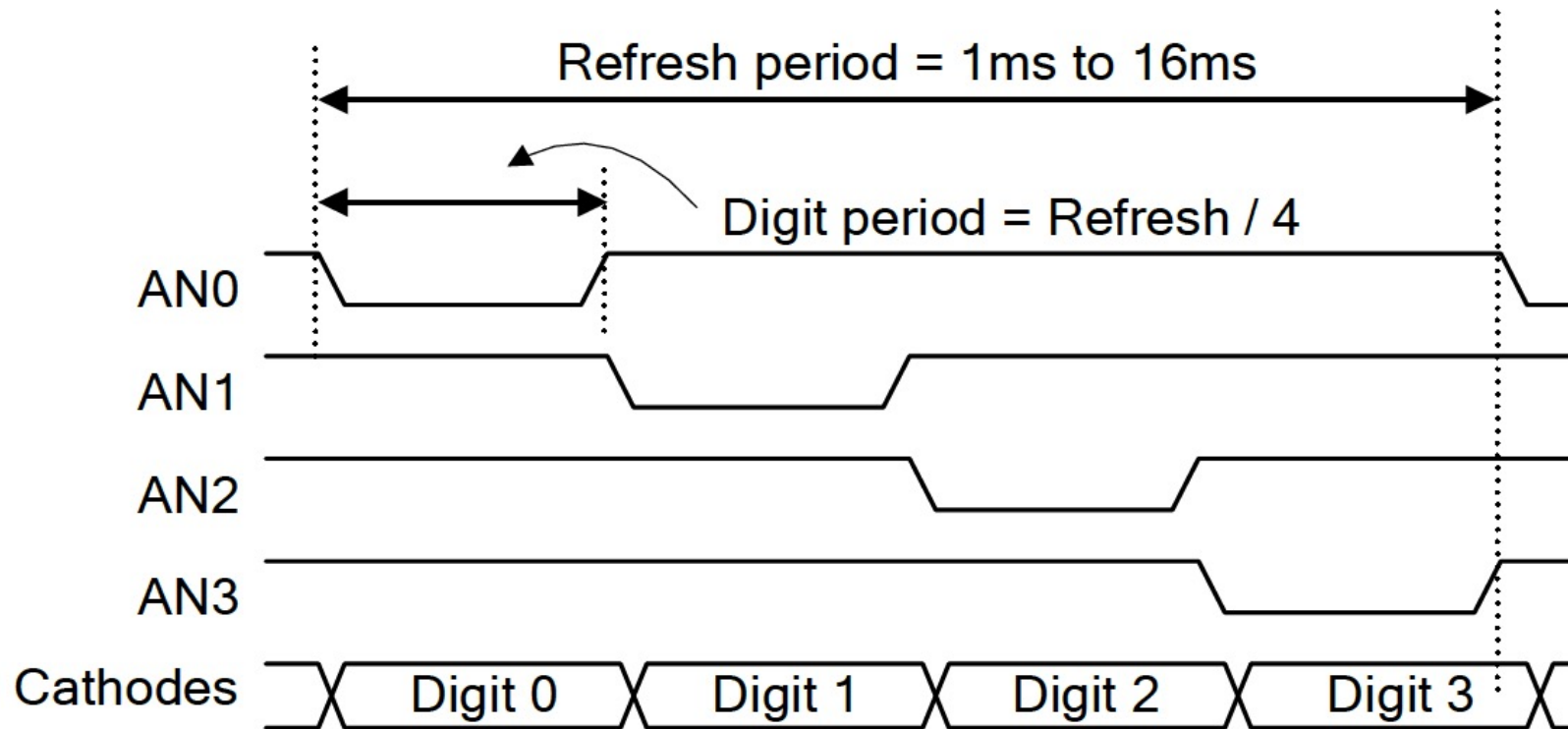
# Timing Diagram to Scan The Four Digits

- The update (or refresh) rate should be  $> 45\text{Hz}$ 
  - ◆ Or a flicker occurs
  - ◆ Typically, the four digits should be driven once every 1 to 16ms
    - Refresh frequency of  $\sim 1\text{KHz}$  to  $60\text{Hz}$




# Control Example (Only Partial Code Segment)

```
always @(posedge clk) begin
  case (DIGIT)
    4'b1110: begin
      value = BCD1;
      DIGIT = 4'b1101;
    end
    4'b1101: begin
      value = BCD2;
      DIGIT = 4'b1011;
    end
    4'b1011: begin
      value = BCD3;
      DIGIT = 4'b0111;
    end
    4'b0111: begin
      value = BCD0;
      DIGIT = 4'b1110;
    end
    default: begin
      value = BCD0;
      DIGIT = 4'b1110;
    end
  endcase
end
```

```
always @* begin
  case (value)
    GFE_DCBA
    4'd0: DISPLAY = 7'b100_0000;
    4'd1: DISPLAY = 7'b111_1001;
    4'd2: DISPLAY = 7'b010_0100;
    4'd3: DISPLAY = 7'b011_0000;
    4'd4: DISPLAY = 7'b001_1001;
    4'd5: DISPLAY = 7'b001_0010;
    4'd6: DISPLAY = 7'b000_0010;
    4'd7: DISPLAY = 7'b111_1000;
    4'd8: DISPLAY = 7'b000_0000;
    4'd9: DISPLAY = 7'b001_0000;
    default: DISPLAY = 7'b111_1111;
  endcase
end
```

 
# Discussion

- ⦿ The sample code is not necessarily the best style
- ⦿ Do not forget the decimal point: DP (V7)
  - ◆ Try to control it
- ⦿ How about the middle “colon”?
- ⦿ How about characters other than decimal digits?






# Other Variations

 

# 14-Segment Display Codes

 


1234567890 .: / ( " \* 1 7 ' )  
0:00  
A B C D E F G H I J K L M N O P Q R S T U V W X Y Z  
A b c d E F 9 h i j k l m n o P Q r S t u v w x y z

# Pushbuttons & Debounce Circuit


# Five Pushbuttons (1/2)

- Arranged in a plus-sign configuration in the demo board
- Momentary** switches
  - Normally generate a **low (0)** output when they are at rest
  - High (1)** output only when they are pressed

Symbol	Pin
BTNU	T18
BTND	U17
BTNL	W19
BTNR	T17
BTNC	U18

 


# Five Pushbuttons (2/2)

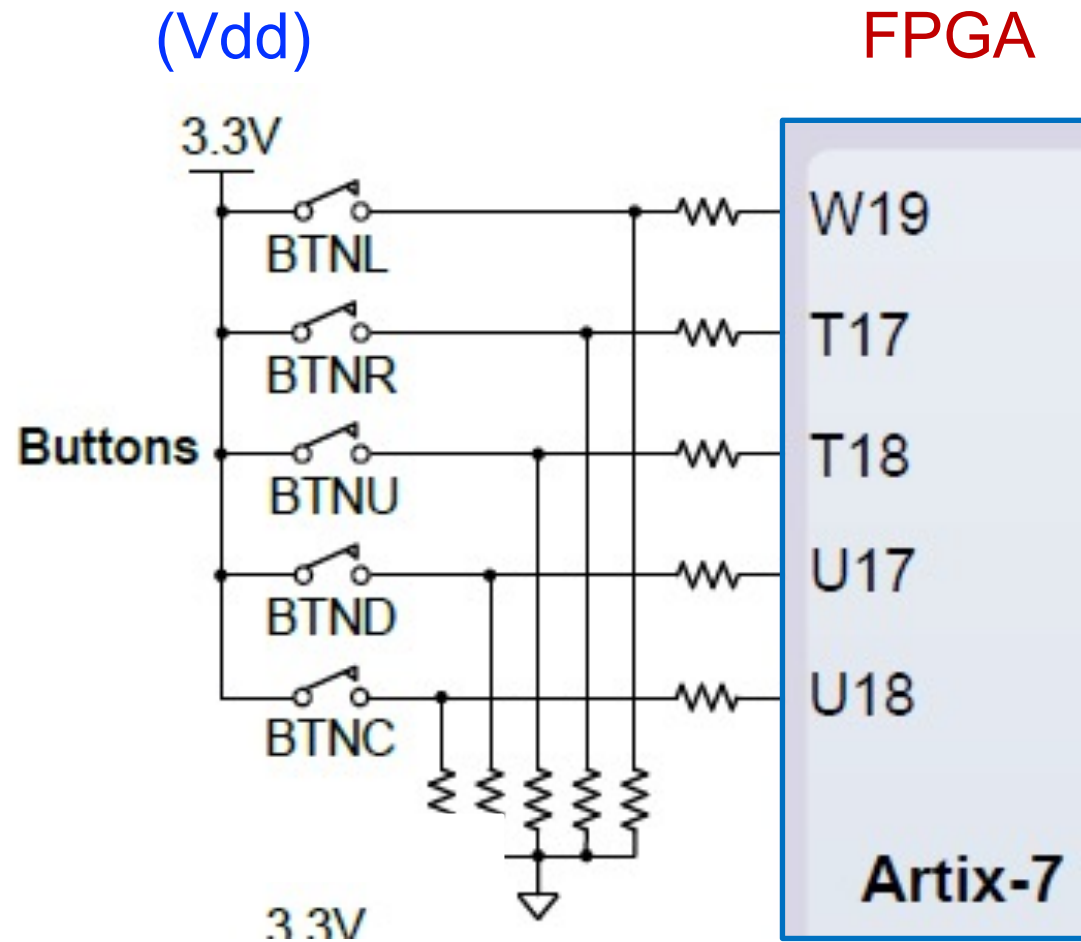


# Switch Contact Bounce

- ⦿ Pushbutton contains a metal spring
  - ◆ When it is pressed and released, the switch contact will bounce several times before stabilizing
  - ◆ A random number of unwanted signal pulses
  - ◆ They are in the  $\mu\text{s}$  range
  - ◆ But the FPGA is sensitive to pulses down to  $\text{ns}$  range
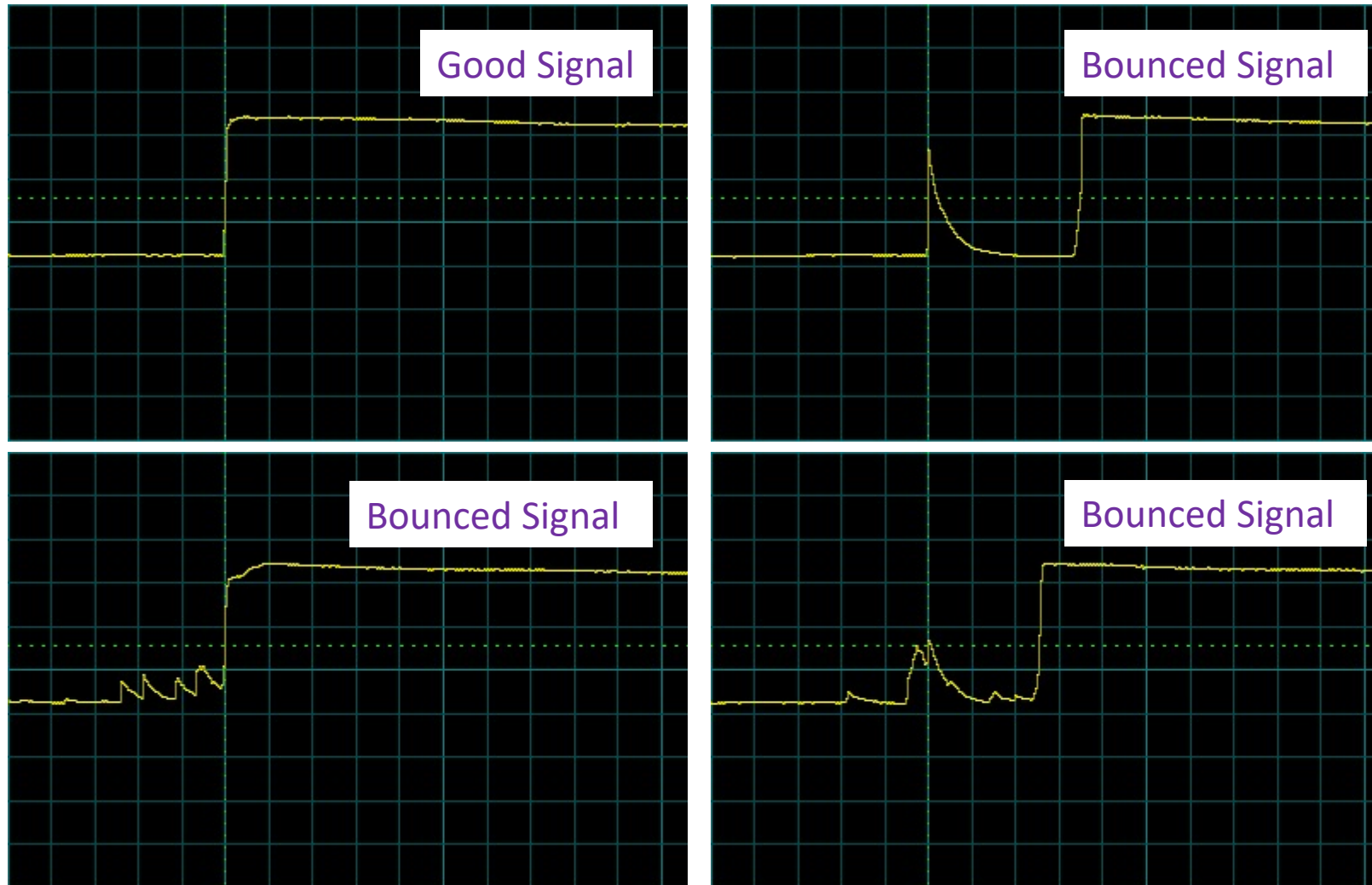
# Possible Ground Bounces When Pushing A Button



# Pushbutton Debounce

 



# Verilog Code of Debounce Circuit

```
module debounce (pb_debounced, pb, clk);

    output pb_debounced; // output after being debounced
    input  pb;           // input from a pushbutton
    input  clk;

    reg [3:0] shift_reg; // use shift_reg to filter the bounce

    always @(posedge clk)
        begin
            shift_reg[3:1] <= shift_reg[2:0];
            shift_reg[0] <= pb;
        end


    assign pb_debounced = ((shift_reg == 4'b1111) ? 1'b1 : 1'b0);

endmodule
```


# One-Pulse Generator
 
# One-Pulse Generator

- ⦿ When a pushbutton is pressed for a short moment
  - ◆ The time to turn on the switch is usually much longer (in ms range) than one clock period (in  $\mu\text{s}$  or ns range)
  - ◆ The circuit will “see” that we are supplying a string of ones as the input
- ⦿ A one-pulse circuit generates only a one-clock-period-long pulse every time a pushbutton is pressed
  - ◆ Independent of the actual time period that the pushbutton was pressed



# Block Diagram of One-Pulse Generator

 

## Inputs

- ◆ pb\_debounced: debounced pushbutton signal
- ◆ clk: the same clock to the circuit
- ◆ rst: reset

## Output

- ◆ pb\_1pulse: high for only one clock cycle when the pushbutton is pressed


# Block Diagram and Waveforms

pb\_debounced

pb\_debounced\_delay

~pb\_debounced\_delay

pb\_1pulse

 

pb\_debounced  
pb\_1pulse  
clk



# Sample Verilog Code

## (Do you need the reset signal?)

```
module onepulse (pb_debounced, clk, pb_1pulse);
  input  pb_debounced;
  input  clk;
  output pb_1pulse;
  reg    pb_1pulse;
  reg    pb_debounced_delay;

  always @(posedge clk) begin
    if (pb_debounced == 1'b1 & pb_debounced_delay == 1'b0)
      pb_1pulse <= 1'b1;
    else
      pb_1pulse <= 1'b0;

    pb_debounced_delay <= pb_debounced;
  end
endmodule
```


# Alternative One-Pulse Generator

```
module onepulse (  
    input wire rst,  
    input wire clk,  
    input wire pb_debounced,  
    output reg pb_1pulse  
);  
    // internal registers  
    reg pb_1pulse_next;  
    reg pb_debounced_delay;  
  
    always @* begin  
        pb_1pulse_next = pb_debounced  
            & ~pb_debounced_delay;  
    end
```

```
    always @(posedge clk, posedge rst)  
    begin  
        if (rst == 1'b1) begin  
            pb_1pulse <= 1'b0;  
            pb_debounced_delay <= 1'b0;  
        end else begin  
            pb_1pulse <= pb_1pulse_next;  
            pb_debounced_delay <= pb_debounced;  
        end  
    end  
endmodule
```
 
# Simulation of One-Pulse Generator

- You may observe the timing
  - ◆ Sequential behavior:  
A DFF introduces one-cycle delay





# Summary

- Refresh rate of the 7-segment → smoothness of the display
- Every input from the pushbutton
  - ◆ Should be properly processed with the debouncing **and/or** one-pulse converters
  - ◆ Except the reset signal (why?)
- Again, clock rate of the debounce/on-pulse circuits → smoothness of the input response