



EECS 2070 02 Fall 2021

Improper Coding Styles

黃稚存

Chih-Tsun Huang

cthuang@cs.nthu.edu.tw



國立清華大學
資訊工程學系

Lecture 09

聲明

- ◎ 本課程之內容 (包括但不限於教材、影片、圖片、檔案資料等)，僅供修課學生個人合理使用，非經授課教師同意，不得以任何形式轉載、重製、散布、公開播送、出版或發行本影片內容 (例如將課程內容放置公開平台上，如 Facebook, Instagram, YouTube, Twitter, Google Drive, Dropbox 等等)。如有侵權行為，需自負法律責任。

Inferring Latch

- ⦿ Perhaps the most common mistakes
- ⦿ Latch is a sequential element
 - ◆ In modern synchronous digital designs, latch is not recommended
 - ◆ Flip-flop is preferred
- ⦿ Improper coding style will introduce latches into combinational blocks

Inferred Latches in Combinational Circuits (1/2)

- ⦿ Incomplete sensitivity list in combinational circuits

```
always @(a or b) begin  
    sum = a + b + cin;  
end
```

```
always @(b, c) begin  
    if (select) a = b;  
    else a = c;  
end
```

- ⦿ Use `always @*` or `always @(*)` instead

Inferred Latches in Combinational Circuits (2/2)

- ⦿ Incomplete if-else statement → inferring **latch!**

```
X always @*  
    if (en)  q = d + 1;
```


- ⦿ Combinational block must have

- ◆ Complete if-else statement

```
always @*  
    if (en)  q = d + 1;  
    else    q = 0;
```

- ◆ Or always specify a **default value** to a variable
 
```
always @* begin  
    q = 0;  
    if (en)  q = d + 1;  
end
```



Incomplete Assignment in Combinational Block



```
always @* begin
    if (a > b) begin
        x = c;
        y = 0;
    end else begin
        y = 1;
    end
end
```

```
always @* begin
    if (a > b) begin
        x = c;
        y = 0;
    end else begin
        x = 0;
        y = 1;
    end
end
```

```
always @* begin
    x = 0;
    y = 1;
    if (a > b) begin
        x = c;
        y = 0;
    end else begin
        x = 0;
        y = 1;
    end
end
```

Incomplete if Statement

- ⦿ The priority encoder fails to check for the possibility of no true inputs

```
module priority (  
    input [3:0] a,  
    output reg [3:0] y);  
    always @*  
  
        if      (a[3]) y = 4'b1000;  
    else if (a[2]) y = 4'b0100;  
    else if (a[1]) y = 4'b0010;  
    else if (a[0]) y = 4'b0001;  
    // else      y = 4'b0000;  
endmodule
```

Warning: Inferred memory devices in process in routine priority line 4 in file 'priority_decoder.v'.

Another Incomplete if Statement

```
always @* begin
    if (enable == 1'b1) begin
        reg_a = A;
        reg_b = B;
    end
    if (swap == 1'b1) begin
        data_a = reg_b;
        data_b = reg_a;
    end else begin
        data_a = reg_a;
        data_b = reg_b;
    end
end
```

*Warning: <location>: **inferring latch(es)** for variable "<name>", which holds its previous value in one or more paths through the always construct*

Incomplete case Statement

```
module divideby3FSM(  
    input clk,  
    input reset,  
    output out);  
    reg [1:0] state, nextstate;  
    parameter S0 = 2'b00;  
    parameter S1 = 2'b01;  
    parameter S2 = 2'b10;  
  
    // State register  
    always @(posedge clk, posedge reset)  
        if (reset) state <= S0;  
        else state <= nextstate;
```

```
    always @(state) // Next state logic  
  
        case (state)  
            S0: nextstate = S1;  
            S1: nextstate = S2;  
            S2: nextstate = S0;  
            // default: nextstate = S0;  
        endcase  
  
    // Output logic  
    assign out = (state == S2);  
endmodule
```

Warning: `<location>`: **inferring latch(es)** for variable "`<name>`", which holds its previous value in one or more paths through the always construct

Combinational Multi-Way Branch

- ◉ Nested if-else statements

```
if (alu_control == 0)
    y = x + z;
else if (alu_control == 1)
    y = x - z;
else if (alu_control == 2)
    y = x * z;
else
    y = 0;
```

- ◉ case statements

```
reg [1:0] alu_control;

case (alu_control)
    2'd0: y = x + z;
    2'd1: y = x - z;
    2'd2: y = x * z;
    default: y = 0;
endcase
```

- ◉ Can replace nested if-else-if statements
- ◉ Can be nested

Complete Assignment for Combinational Circuits

Style A

```
always @* begin
    if (en==1'b1) begin
        if (out == 4'd9) begin
            out_next = 4'b0;
            co = 1'b1;
        end else begin
            out_next = out + 1'b1;
            co = 1'b0;
        end
    end else begin
        out_next = out;
        co = 1'b0;
    end
end
```

Style B


```
always @* begin
    out_next = out;
    co = 1'b0;
    if (en==1'b1) begin
        if (out == 4'd9) begin
            out_next = 4'b0;
            co = 1'b1;
        end else begin
            out_next = out + 1'b1;
        end
    end
end
```

Ex: Ambiguous Output Definition

- out1 is intended to be 1 when state is 0;
out2 to be 1 when state is 1
- ◆ However, the code never sets the outputs low.

```
reg state, out1, out2;  
always @(posedge clk)  
    if (state == 0) begin  
        if (a) state <= 1;  
    end else begin  
        if (~a) state <= 0;  
    end  
  
always @*  
    if (state == 0) out1 = 1;  
    else  
        out2 = 1;
```

Synthesis Results

 

Ex: Ambiguous Output Definition (Correction)

```
reg state, out1, out2;
always @(posedge clk)
  if (state == 0) begin
    if (a) state <= 1;
  end else begin
    if (~a) state <= 0;
  end

always @*
  if (state == 0) begin
    out1 = 1;
    out2 = 0;
  end else begin
    out1 = 0;
    out2 = 1;
  end
endmodule
```

Synthesis Results

