

EECS 2070 02 Fall 2021

Improper Coding Styles

黃稚存

Chih-Tsun Huang

cthuang@cs.nthu.edu.tw



國立清華大學
資訊工程學系

Lecture 08


聲明

- ◎ 本課程之內容 (包括但不限於教材、影片、圖片、檔案資料等)，僅供修課學生個人合理使用，非經授課教師同意，不得以任何形式轉載、重製、散布、公開播送、出版或發行本影片內容 (例如將課程內容放置公開平台上，如 Facebook, Instagram, YouTube, Twitter, Google Drive, Dropbox 等等)。如有侵權行為，需自負法律責任。


Hazards

Hazards (or Glitches)

 
- ⦿ Unwanted switching transients appearing in the **output of a combinational circuit** while its inputs change
- ⦿ Types of hazards (assuming only a single input can change at a time and no other input will change until the circuit has stabilized)



(a) Static 1-hazard


 


(b) Static 0-hazard

 


(c) Dynamic hazards

Hazards (cont)

 
 


 - Function output transits across two implicants
→ Possible hazards



Hazard Eliminating



Covering transitions across implicants

  

Synchronous Design vs. Asynchronous Design


Synchronous Design

● Cycle-based

  

Asynchronous Sequential Circuit

 - Asynchronous sequential circuit is hard to verify



```
always @(posedge en) begin
    ...
```



- We prefer **synchronous**, **single-clock** sequential blocks


Gated Clock

- Introduces unexpected glitches to the clock signal
- Also makes the circuit asynchronous

```
always @(clk or en) begin  
    ...
```


```
always @* begin  
    ...  
    condition = clk & en;
```
 
```
always @* begin  
    ...  
    if (clk == 1) ...
```





Dual Clock-edge Triggered

 - Reduces the effective clock period
- Runs into trouble when the duty cycle of the clock isn't 50% as the ideal case


 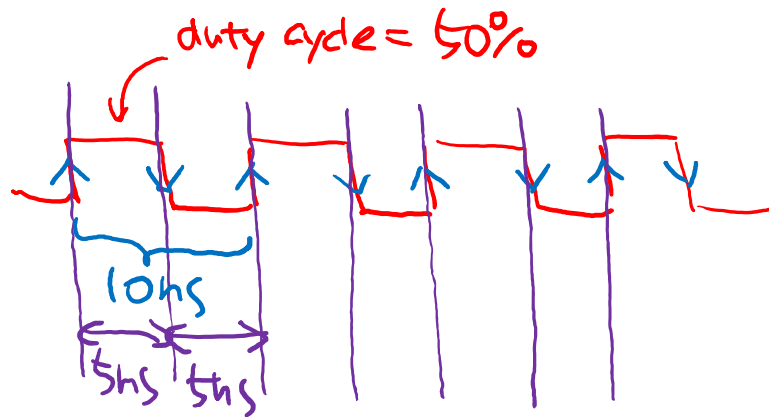
```
always @(posedge clk or negedge clk) begin  
    ...  
end
```



Mixed Edge and Level Triggered

- ⦿ Mixed edge-triggered and level-sensitive control in an always block

```
always @(addr or posedge clk) begin
```

```
...
```

- ◆ Syntax error for old Verilog simulator
- ◆ Acceptable now, but restricted to

```
always @(posedge clk or reset)
```

```
|||
```

```
always @(posedge clk or posedge reset)
```

X or Z for Outputs of Combinational Circuits

- ⦿ Incorrect connection of IO ports
 - ◆ Width mismatch
 - ◆ Floating input
 - ▣ Undefined reg-type signal: X
 - ▣ Unconnected wire-type signal: Z
- ⦿ Sometimes designers assign outputs as an X for invalid inputs on purpose
 - ◆ Not recommended for synthesizable design
 - ◆ X only exists in simulation, not in realistic world

```
case
    ...
    default: out = 1'bx;
endcase
```